

# Chapter 4 Fault Simulation

錯誤模擬



# Outline



- Introduction to Fault Simulation
- Fault Simulation for Combinational Circuits
- Techniques for Sequential Circuits
- Fault Grading

# What is Fault Simulation?



Given :

- **A circuit**
- **A test (sequence of test vectors)**
- **A fault model**

Determine:


- **Fault coverage (the fraction of modeled faults detected)**
- **Undetected faults**

# Applications of Fault Simulation



- Determine fault coverage of a given test sequence
  - Measure test quality by fault coverage
- Determine undetected faults for test generation
- Construct fault dictionary for diagnosis
  - Use a fault simulator to compute & store the response for every fault
  - If the output response of the circuit under test matches any of the response in the fault dictionary, the fault location is identified

# Conceptual Fault Simulation

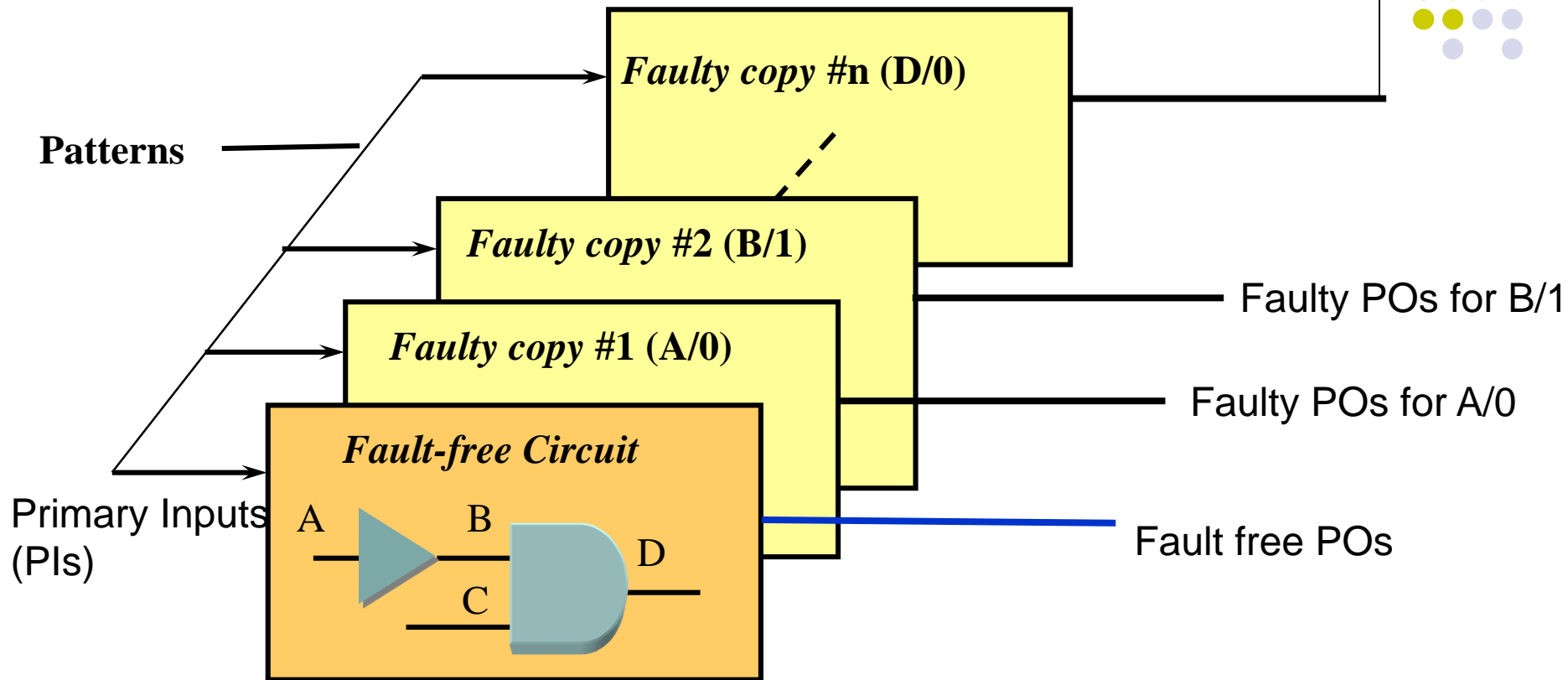

- One logic simulation for every fault-free and faulty circuits
- Complexity  $\sim O(F \times P \times G)$ 
  - $F$ : # of faults;  $P$ : # of patterns;  $G$ : # of gates
- A simple technique: fault dropping.

# Fault Simulation Techniques



- Parallel-Fault (Single-Pattern) Simulation
- Deductive Fault Simulation
- Concurrent Fault Simulation
- Parallel-Pattern Single-Fault Simulation
- Critical Path Tracing

# Parallel Fault Simulation



- Simulate multiple circuits at a time
  - The inherent parallel operation of computer words to simulate faulty circuits in parallel with fault-free circuit
  - The number of faulty circuits (one for each fault) to be simultaneously processed is limited by the word length, e.g., 32 circuits for a 32-bit computer
- The fault-free logic simulation is repeated for each pass
  - This can be avoided by storing fault-free values in another word.

# Speedup of Parallel Fault Simulation



- There are extra costs associated with parallel fault simulation, so the speed up is only sub-linear.
  - An event, a value-change of a single fault or fault-free circuit leads to the computation of the entire word
  - A proper **fault grouping** is needed.
    - Group *similar* faults in the same simulation




# Example: Parallel Fault Simulation



- Assume 4-bit computer words
- Consider three faults: J s-a-0, B s-a-1, and F s-a-0
- Bit allocation: 

<b>A/0</b>	<b>B/1</b>	<b>F/0</b>	<b>FF</b>
------------	------------	------------	-----------


 ← Fault free bit

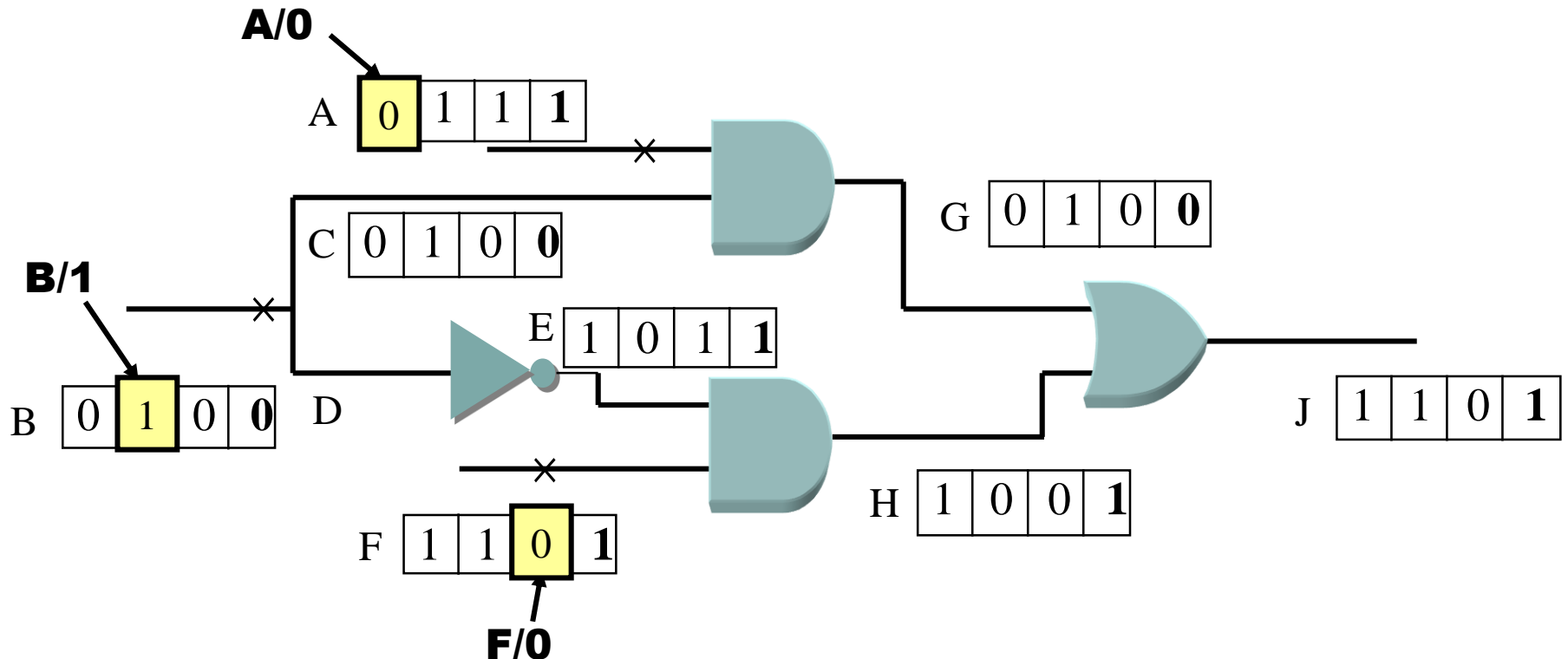
 
# Fault Injection by Circuit Modeling



- By changing only the circuits, we can use a parallel logic simulator to implement a parallel fault simulation.



# Parallel Fault Simulation – Summary




- Most effective for
  - Interconnected logic gate netlist
  - Stuck-at faults
  - Two-valued logic
- Little resource required
  - Easy to implement
  - Fixed and low memory requirement
- Some extra cost
  - Faults injected in the same word may not generate the same events.
  - The fault-free circuit is simulated in each pass.

 
# Fault List in Deductive Fault Simulation



- Represent the fault list of a signal with a set.
- A fault is in a fault list of a targeted signal if
  - The fault changes the fault-free value of the signal, or
  - The fault is propagated to the signal



Fault list before simulation

 


Fault list after logic simulation

# Propagation of Fault List



- Create an initial fault list at every signal (inject collapsed faults)
- Propagate fault list starting from PIs.
- Propagate through gates level by level (logic deduction)
  - Propagation rules are set operations and depends only on gate type and its input values.
- A fault is detected if it appears in the fault list of a primary output.

# An Example of Fault List Propagation

 

- Input  $a = 0, b = 1$
- $a = 0 \rightarrow L_a = \{a_1\}$ 
  - $a_1$ :  $a$  stuck-at-1
- $b_0$  in  $L_b$  is not propagated to  $L_c$  because  $a = 0$  is the controlling value.

# Rule of Fault List Propagation



	<i>a</i>	<i>b</i>	<i>z</i>	Output fault list
AND	0	0	0	$\{L_a \cap L_b\} \cup z_1$
	0	1	0	$\{L_a - L_b\} \cup z_1$
	1	0	0	$\{L_b - L_a\} \cup z_1$
	1	1	1	$\{L_a \cup L_b\} \cup z_0$
OR	0	0	0	$\{L_a \cup L_b\} \cup z_1$
	0	1	1	$\{L_b - L_a\} \cup z_0$
	1	0	1	$\{L_a - L_b\} \cup z_0$
	1	1	0	$\{L_a \cap L_b\} \cup z_0$
NOT	0		1	$L_a \cup z_0$
	1		0	$L_a \cup z_1$



# Fault List Propagation Rule

- Notations:
  - Let  $I$  be the set of inputs of a gate  $Z$  with a controlling value  $c$  and inversion  $i$  (i.e.,  $i$  is 0 for AND, OR and 1 for NAND, NOR)
  - Let  $C$  be the set of inputs with value  $c$

## Non-controlling case:

$$\text{if } C = \emptyset \text{ then } L_z = \left\{ \bigcup_{j \in I} L_j \right\} \cup \{Z \text{ s-a-}(c \oplus i)\}$$

union

## Controlling cases:

$$\text{else } L_z = \left\{ \bigcap_{j \in C} L_j \right\} - \left\{ \bigcup_{j \in I-C} L_j \right\} \cup \{Z \text{ s-a-}(\bar{c} \oplus i)\}$$

intersection





# A Generalized Propagation Rule – Cont'd



- If no input has value  $c$ , any fault effect on any input propagates to the output.
- If some inputs have value  $c$ , only a fault effect that affects all the inputs with  $c$  without affecting any of the inputs with  $c'$  propagates to the output.
 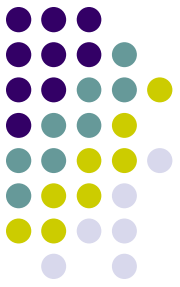
# An Example of Deductive Fault Simulation



$$L_a = \{a_0\}$$

$$L_b = \{b_0\}$$

$$L_c = \{b_0, c_0\}$$


$$L_d = \{b_0, d_0\}$$

$$L_e = L_a \cup L_c \cup \{e_0\} = \{a_0, b_0, c_0, e_0\}$$

$$L_f = \{b_0, d_0, f_1\}$$


$$L_g = \{L_e - L_f\} \cup \{g_0\} = \{a_0, c_0, e_0, g_0\}$$
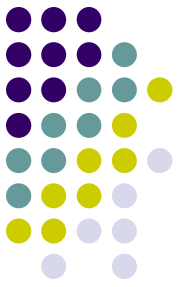
# The Deductive Fault Simulation Algorithm





- **Levelize the circuit from PIs to POs.**
- **Step 1: Read a test vector.**
- **Step 2: Perform logic simulation.**
- **Step 3: Perform fault list propagation.**
- **Step 4: Determine detected faults.**
- **Goto step 1**

# Fault Collapsing


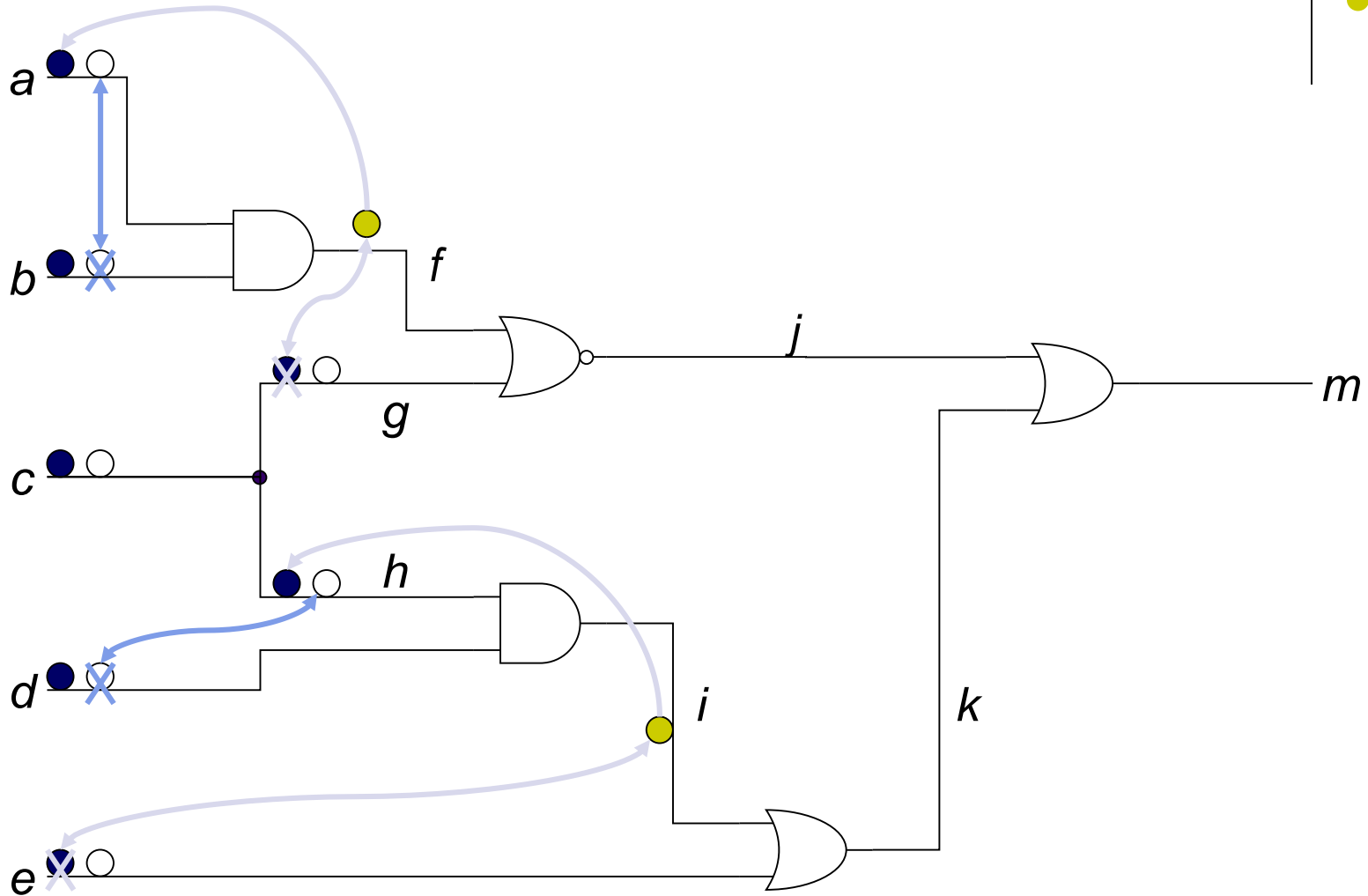


Collapsed fault list:  $\{a_0, a_1, b_1, c_0, c_1, d_1, e_0, g_0, h_0, h_1\}$



# Logic Simulation

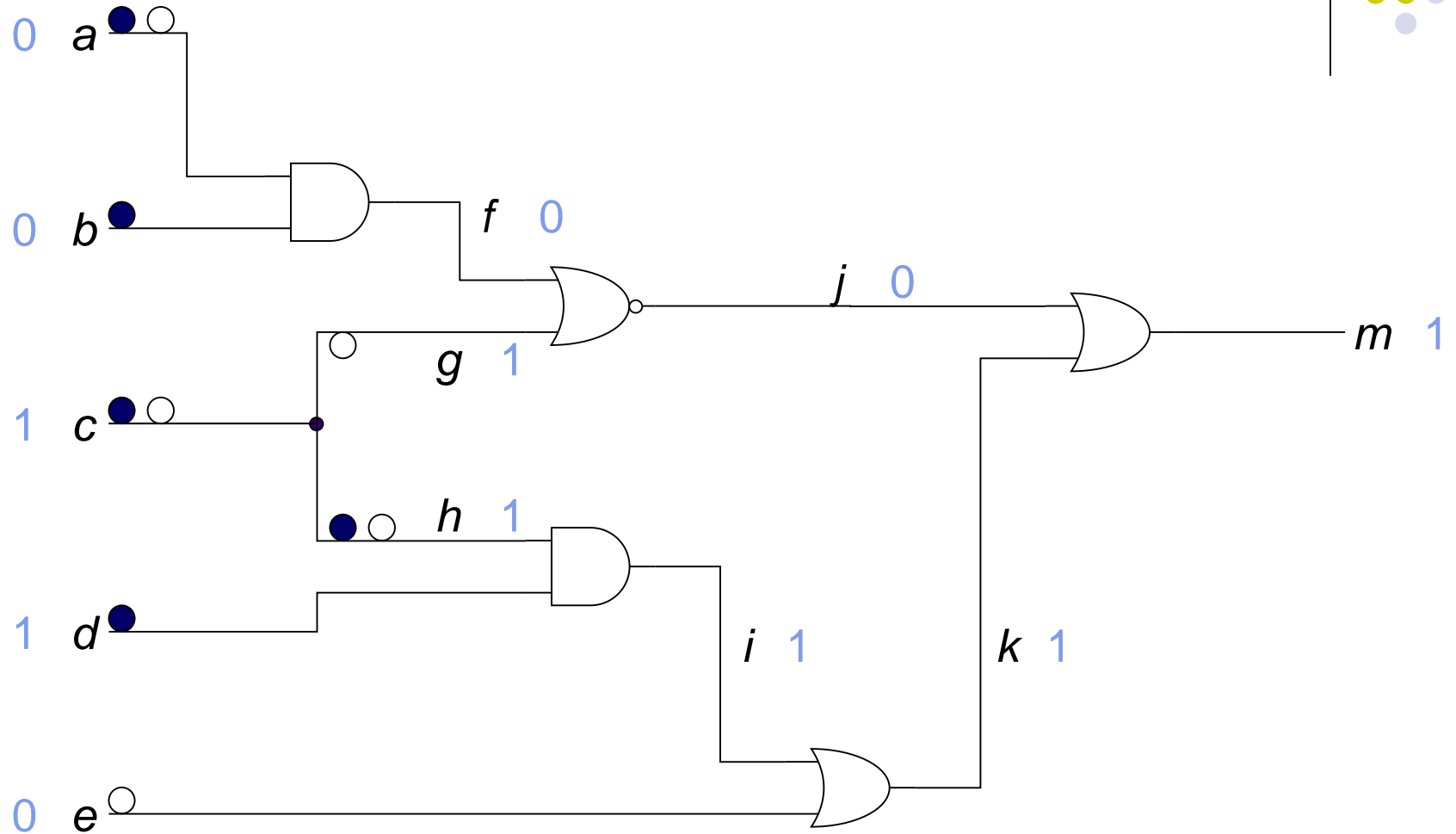 



# Fault List Propagation

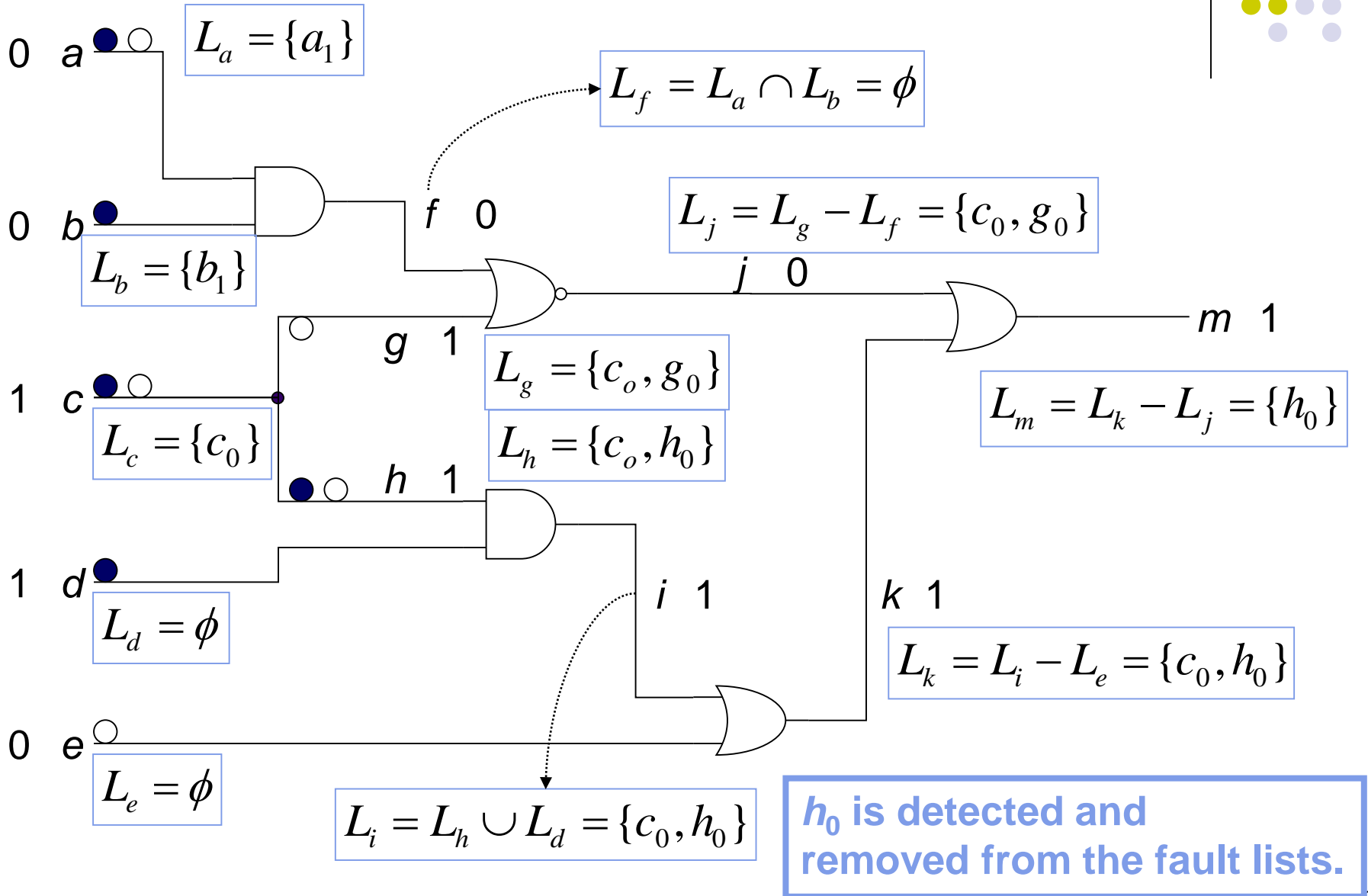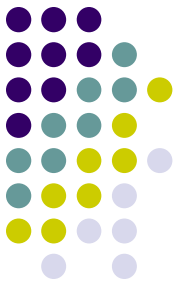

# Apply the Next Vector

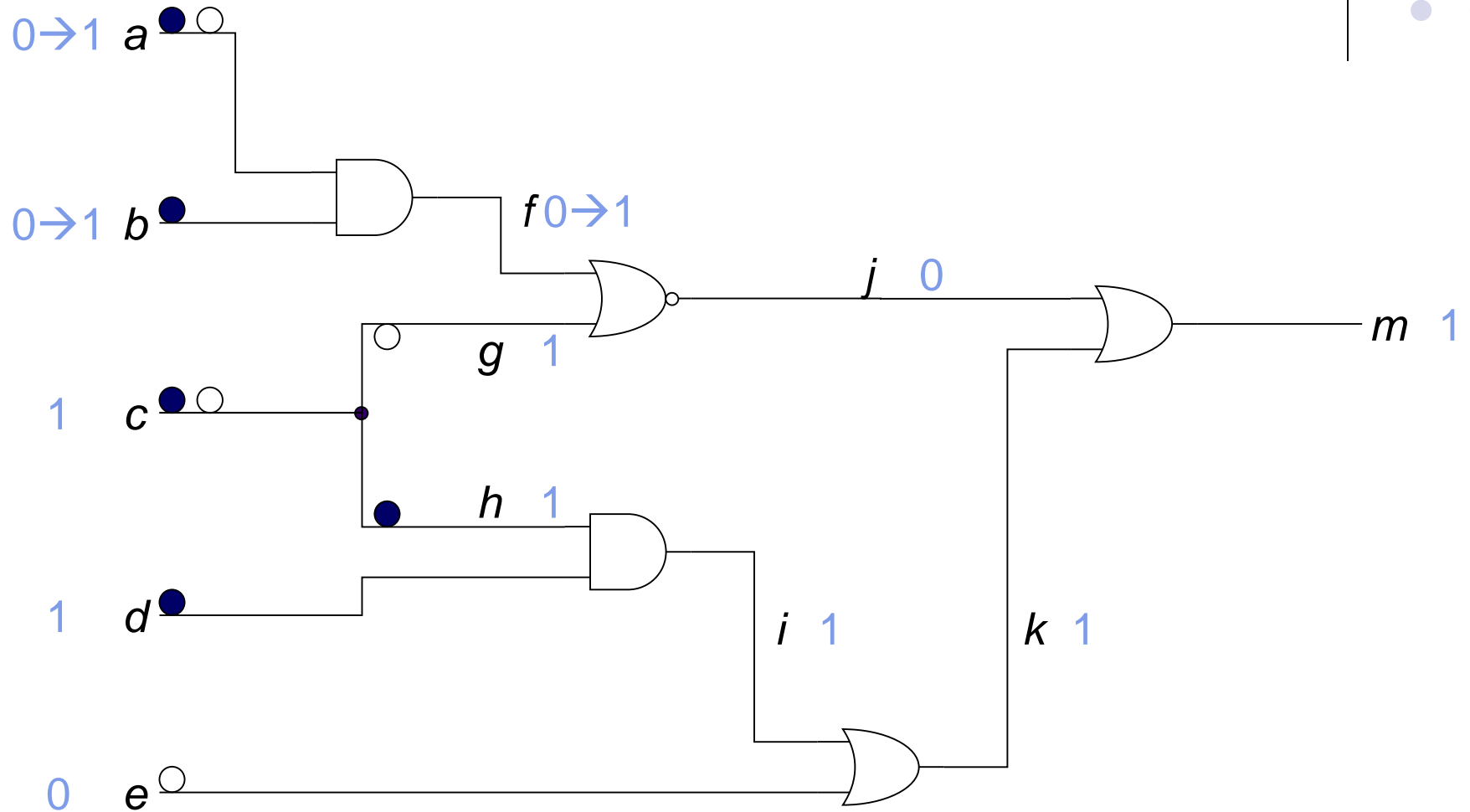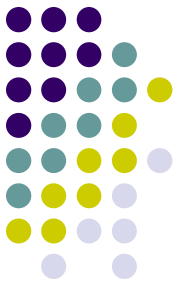

# Fault List Propagation

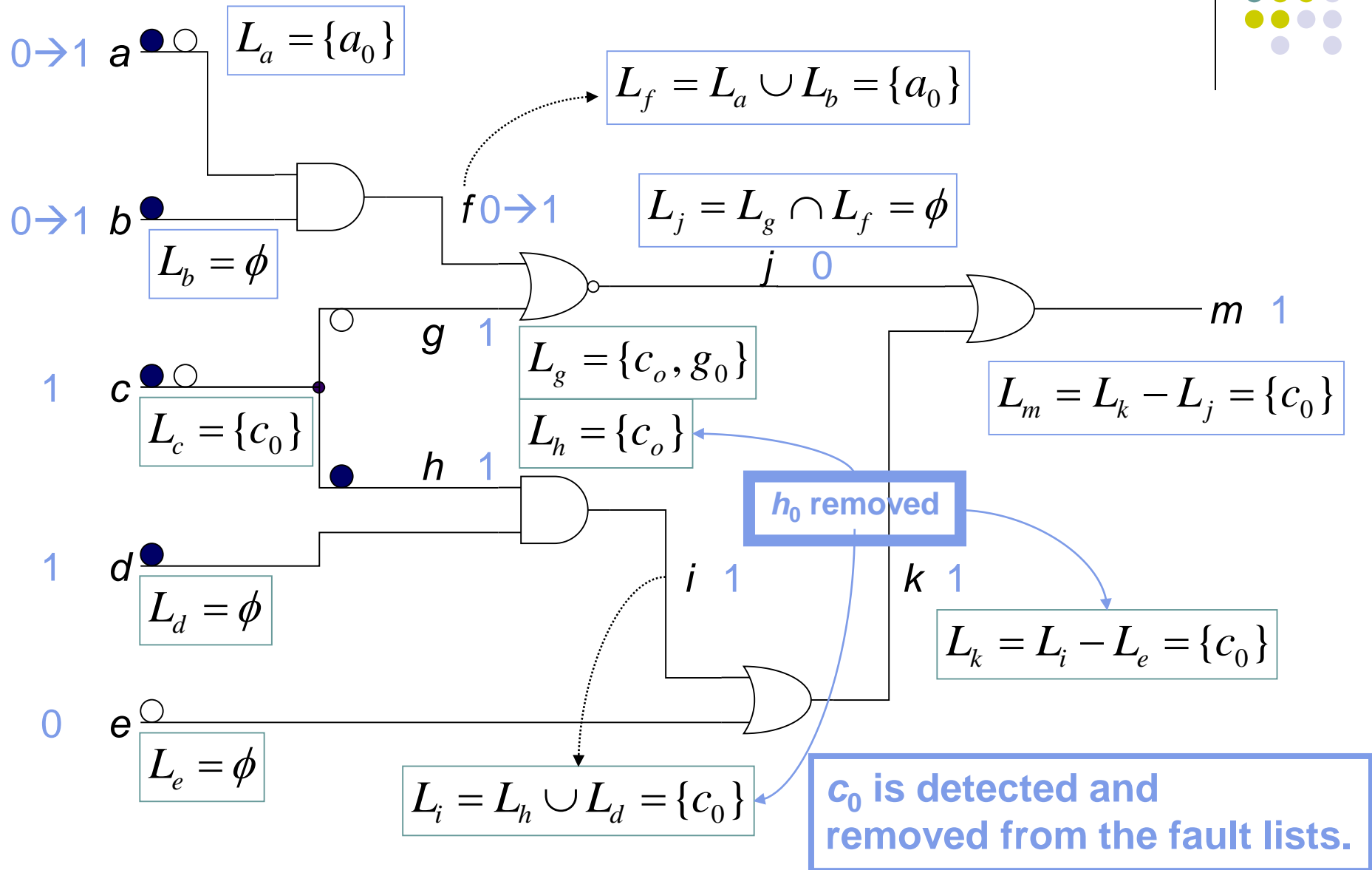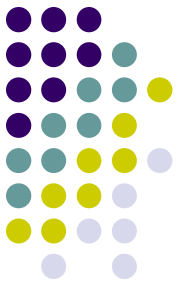



# Faults in Concurrent Fault Simulation




- Every signal uses a data structure called fault list, to store a list of faulty gates
  - Each faulty gate stores the status of a fault
    1. If a fault is activated (i.e., the signal is the fault site) or
    2. Propagated to this gate.
 
# Faulty Gate Structure in Concurrent Fault Simulation



- Each element in the fault list contains
  - Fault index
    - For example, a0 in the following
  - Fault states: input and output values associated with the fault



This faulty gate (for a stuck-at 0) changes a faulty input to 0 and output to 0.

# Concurrent Fault Simulation



- An extension of event-driven simulation
  - Event-driven simulation for both fault free events and faulty events.
- Events in concurrent fault simulation
  - **Fault-free event:** (signal, value)
    - Generated by PI changes
    - Applied to both fault free and faulty circuits.
  - **Faulty event:** (fault index, signal, value)
    - Generated by faults
    - Applied only to the faulty circuit.

# Maintain the Faulty List




- After fault-free and faulty event propagation, an element is in the list iff the I/O values of the faulty circuit are different from the fault-free values.
- A faulty gate with the same output value as the true circuit is kept,
  - Fault can propagate through multiple paths: we might need to evaluate a faulty gate several times before we know no faulty effects pass
- A local fault (at inputs or outputs of a gate) will be kept in the list even when all its I/O values are the same as those of the fault-free circuit.
  - Note that dropped faults will be deleted.

# Fault Dropping



- We can hash every dropped faults, and process every faulty list to remove dropped faults.
- We can also remove dropped faults at fault site, and remove faulty gates if no fanin faulty list contains the fault.


# Concurrent Fault Simulation – Example

 

 
# Concurrent Simulation - Convergence



$a_0$ ,  $c_0$  and  $e_0$  converge into good gates.




# Concurrent Simulation - Convergence

 




# Concurrent Simulation - Divergence

 

# Concurrent Simulation - Divergence

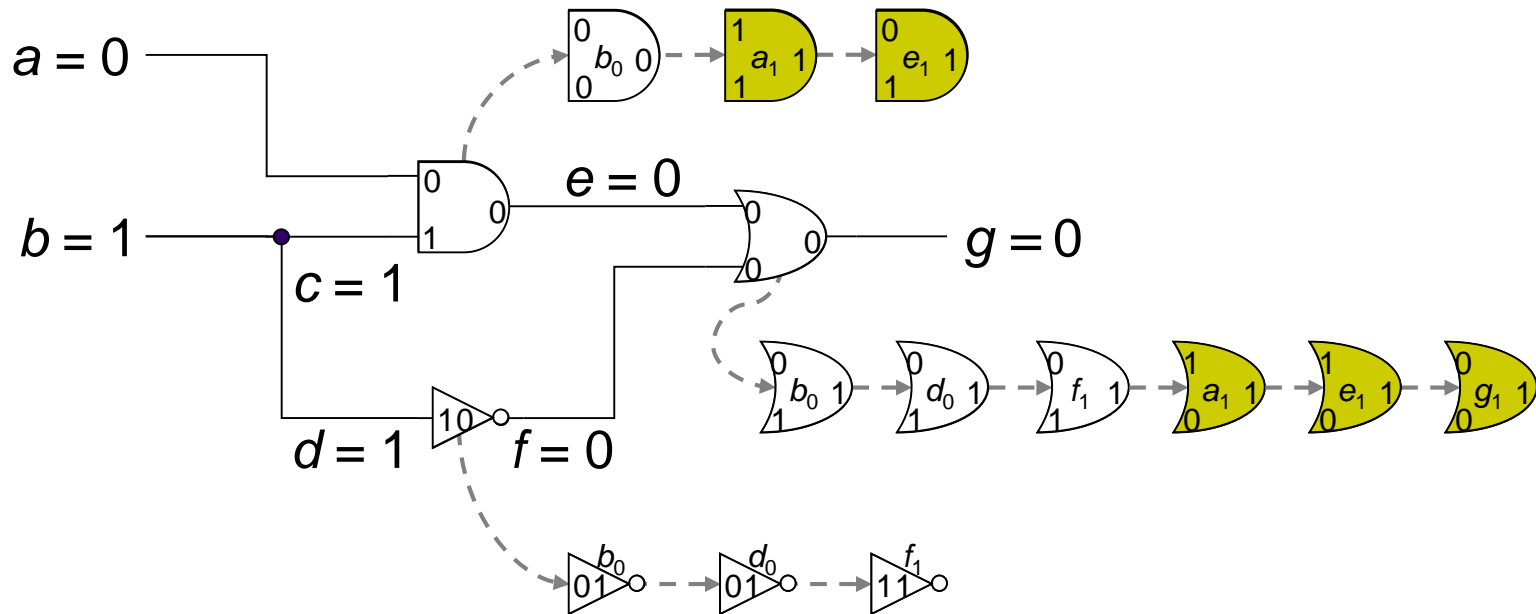

# Disadvantages of Deductive & Concurrent Fault Simulation



- Large memory to record the status of all circuits (fault-free & faulty).
  - Dynamic memory (linked lists)
- Evaluation overhead on the linked lists
  - Comparing fault lists
  - Removing faults
  - Adding faults
- Performance overhead in memory management
- However, concurrent fault simulation handle different fault types and delay of a signal.

# Parallel-Pattern Single-Fault Propagation (PPSFP)




- Use multiple computer words to simulate multiple input patterns.
- It can be based on an event-driven simulation.
- Simple and Extremely Efficient
  - Basis of most modern combinational fault simulators
  - Note that this is mostly the case we use a fault simulator, since ATPG is also limited to combinational circuits.
- It is also applicable to sequential circuits.

# Parallel-Pattern v.s. Parallel-Fault




## Parallel-pattern

(P1, P2, P3 are events by patterns)

 

## Parallel-fault

(F1, F2, F3 are events by faults)

 

- Parallel fault simulation will be more efficient if
  - Faulty events are generated and propagated to POs.
  - Otherwise, events are useless.
- In general, parallel faults generate different events, and they are usually not detected simultaneously by a single PI pattern.
- Parallel pattern simulation is more efficient.


# Re-visit Parallel Fault Simulation




- Bit allocation: 

<b>A/0</b>	<b>B/1</b>	<b>F/0</b>	<b>FF</b>
------------	------------	------------	-----------

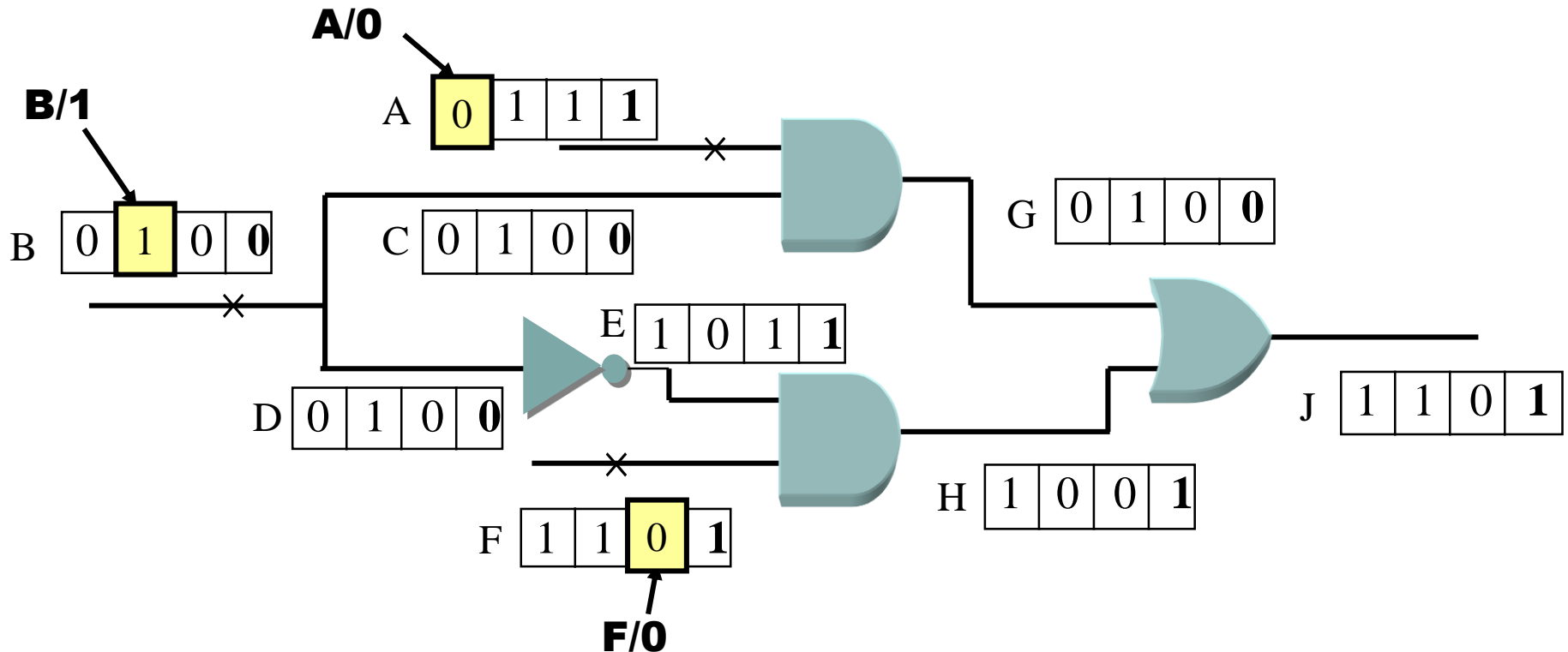 ← Fault free bit
- There are 9 events, but only one fault is detected!




# Example: Parallel Pattern Simulation

 


- Consider one fault F/0 and four patterns: P3,P2,P1,P0
- Bit allocation: 


<b>P3</b>	<b>P2</b>	<b>P1</b>	<b>P0</b>
-----------	-----------	-----------	-----------
- There are only three faulty events!

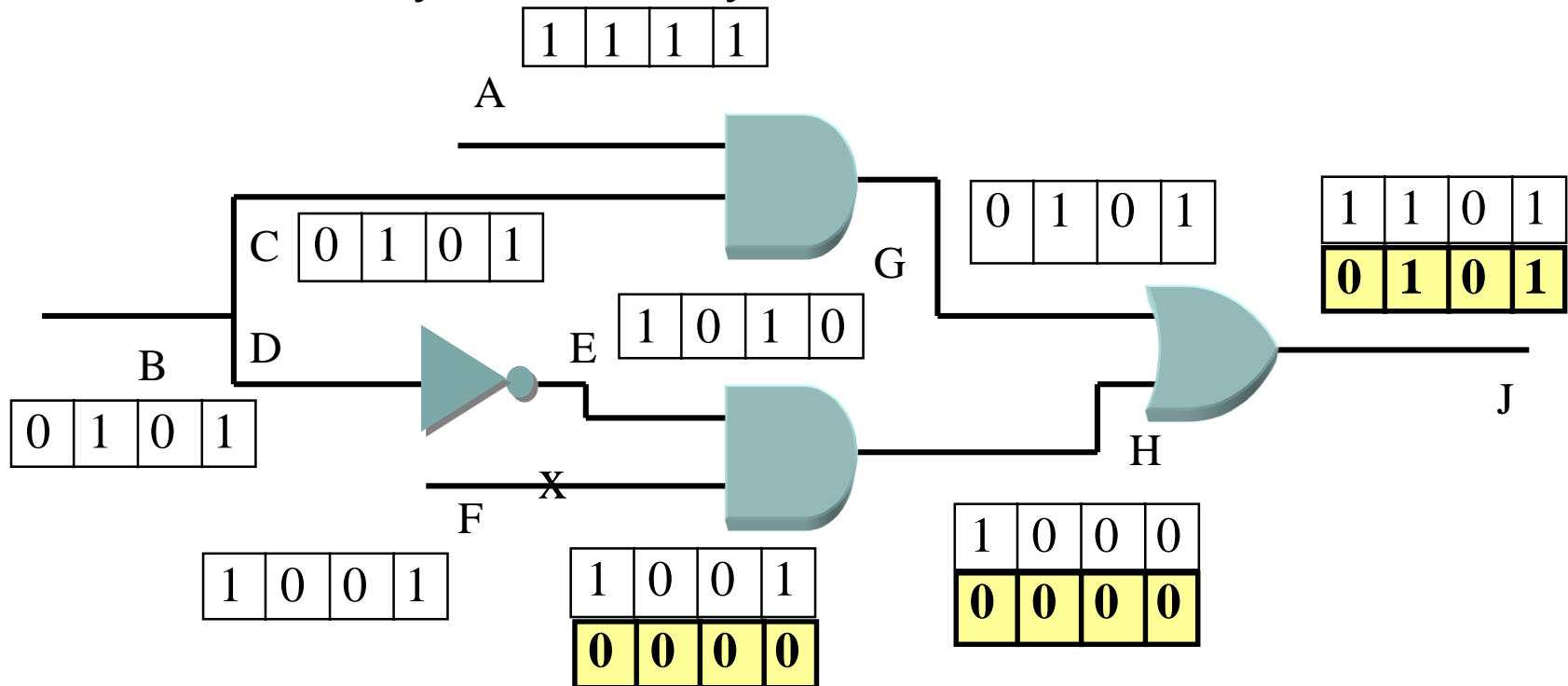

# Critical Path Tracing

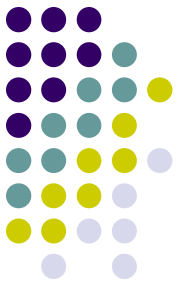

- Find faults detected by a test without simulating all faults.
- The key is to find critical lines in the circuits by tracing from POs.
  - line  $w$  is **critical** for a pattern  $t$  iff  $t$  detects  $w$  stuck-at  $v$ 
    - fault-free value of  $w$  is  $v'$  (under  $t$ )
- Any PO is critical.
- Find whether any inputs of gates to PO are critical recursively
  - If a line of a gate output is critical, the critical property can be transferred to its sensitive inputs.
  - A gate input  $i$  is **sensitive** if complementing the value of  $i$  changes the value of the gate output

 



# Algorithm of Critical Path Tracing




- For a fanout-free circuit,
  - Critical lines can be determined by backward traversing the sensitive gate inputs from PO's, in linear time
  - In general, special processing has to be done for stems
- General Critical path tracing:
  1. Fault-free simulation
  2. Extract single-PO logic cones and process each cone
    1. Process stems with highest levels
    2. If **the stem is critical**, mark critical lines in the fanout free region according to the sensitivity properties.
 
# Critical Property of a Stem



- A stem is critical
  - If all the capture lines are critical.
  - All sensitized paths to POs for the stem pass through the capture lines (dominator).
- Note that this is only an approximation!




# Problems of Critical Path Tracing




- The fault coverage by complete critical path tracing is approximate.
  - Self-masking paths lead to over-estimation
  - Multiple-path sensitization leads to under-estimation.
- Not very useful as a standalone simulator.
- Applied to individual fanout-free regions
  - Note that stem faults are only simulated to its dominators and then faults at dominators become representatives.


# Self-masking Paths

 

 - Detected faults in the fanout-free region: {J/0, H/0, G/1, F/0, E/0, D/1, C/1}
- **Stem criticality** is hard to infer from branches.
  - For example, is B/1 detectable by the given pattern?
- **B/1 is not detectable** even though both C and D are critical, because their effects cancel out each other at gate J
  - **Self masking when** paths go through different inversions



# Multiple Path Sensitization

 

**Both C and D are not critical, yet B is critical and B/0 can be detected at J by multiple path sensitization.**

# Techniques for Sequential Fault Simulation




- Fault simulation without restoration
- Fault grouping for parallel fault simulation
- Single Event Faults
- Management of hypertrophic faults
- Parallel pattern simulation for sequential circuits
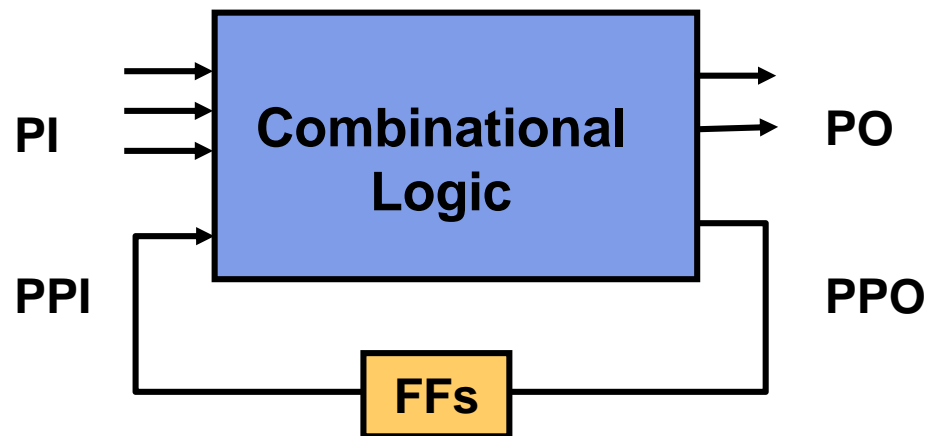
# Sequential Circuit Model



- For sequential circuits, a Huffman model will be used for the following discussion.




PPI: pseudo primary inputs (i.e., outputs of flip-flops)  
PPO: pseudo primary outputs (i.e., inputs of flip-flops)
 
# Faulty State in Sequential Simulation



- Faults will propagate to FF's
  - Need to record faulty states
  - Like multiple faults



Ex: Input Sequence (P1, P2, P3)

State Sequence (S0 → S1 → S2 → S3)




# Fault Simulation without Restoration




- A new fault can be simulated without restoring status of previous fault status to fault-free value.
  - To store and restore fault-free values is inefficient
- Techniques for simulation without restoration
  - Only two sets of values are retained at each gate: one for fault-free and one for faulty ones.
  - Each active fault at any given time is given a unique identifier (ID).
    - Only faulty values with the same ID are used.
    - Otherwise, true values are used.
- Efficient in both time and memory space[ROOFS89].

# Simulation without Restoration

 

 With Restoration: Effect of F1 is cleared before simulating F2




Without Restoration: F2 is simulated right over effect of F1

# Fault Grouping




- Faults with coincident events can be grouped together for parallel simulation.
  - Static fault grouping
    - Based on circuit structure such as fan-in cone, depth-first path from POs.
  - Dynamic fault grouping
    - Fault grouped according to the similarity of faulty states
    - At the beginning of each time frame, faults are dynamically re-grouped for effective usage of all bits in a word
 
# Fault Grouping in Parallel Fault Simulation



- The lower grouping case is evidently more desirable than the upper case because similar faulty events are simulated in parallel.
- Similar events have higher probability to be
  - dropped together
  - detected together
- Distinct faulty events will cause unnecessary simulation of inactive faults

# Single Event Faults

 

● For circuit in a time frame, faults are classified into **single event faults**, e.g. ,  $F1$ , and **multiple event faults**, e.g.,  $F2$ .

- Single event faults are those whose effects originate only from the fault sites of the current time frame.
- Sophisticated combinational techniques, such as **simulate-to-dominators**, can then be applied with significant performance improvement.
- Only single-event stem faults or multiple-event faults are parallel-simulated.
- [HOPE DAC92]

# Hypertrophic Faults




- A hypertrophic fault is a fault that diverges from the fault-free circuit with a large number of X's
  - Usually a stuck-at fault occurring at a control line and thus prevents the circuit initialization
  - A small number of hypertrophic faults can account for a large percentage of fault events and CPU time
- These faults are sometimes dropped
  - as **potentially detected faults** to reduce simulation time. (Fault coverage is approximate)
- In parallel fault simulator
  - such as PROOFS, these faults can be simulated in parallel with fault-free circuit with little additional memory while achieving performance close to approximate simulator [HyHOPE IEE Circuits, Devices and Systems 94].

# Parallel Pattern Simulation for Sequential Circuits




- Sequential circuits are state dependent by nature
  - However, many of them have a short memory, which can be exploited by parallelism of sequences or patterns.
- The basic mechanism of both parallel sequence and pattern
  - To initialize unknown FFs as Xs
  - Simulate the circuit and update the FFs by multiple passes.
  - States will converge to the true values eventually.
- The convergence rate (# of passes)
  - Determines the speed of simulation.
  - Usually small compared with the word length
  - Dependent on the circuit as well as the given sequence.

# Sequential Simulation Example

 



# Parallel Sequential Simulation Example

 


A=0100  
A=0100  
A=0100

B=1X11  
B=1011  
B=1011

C=1X11X  
C=1011X  
C=1011X

Converge for three passes

 
# Parallel Sequential Simulation with Look-ahead Heuristic



Usually most state variables stay the same, so they are good guess for next simulation.

# Parallel Sequential Simulation

## Example (If Look-ahead not used)

 



A=1100  
A=1100  
A=1100

B=XX11  
B=X011  
B=1011

C=XX111  
C=X0111  
C=10111

Also need three passes
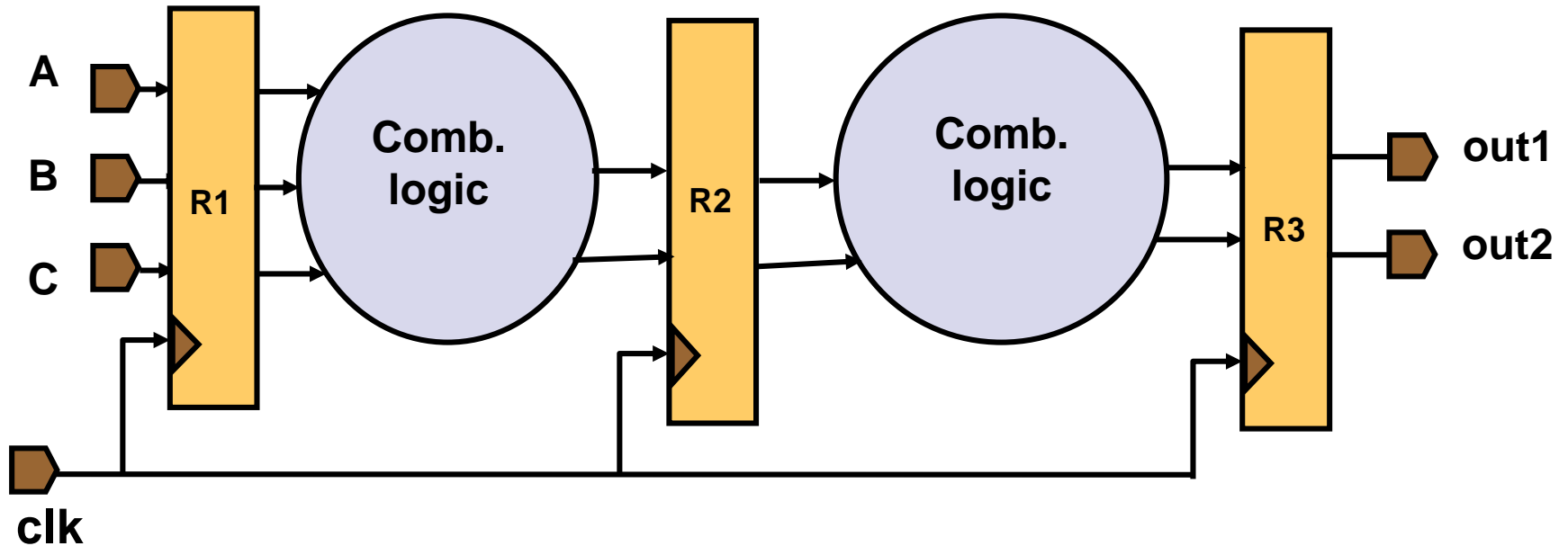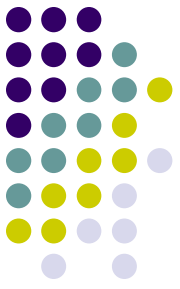
# An Extreme Example of Short-Memory Circuit



**A pipelined data-path**

Because there is no feedback, every patterns can be simulated independently.

# Fault Grading



- Approximate fault coverage
  - Can be obtained in much shorter computational time than regular fault simulation.
  - Not suitable for high fault coverage.
    - It often occurs that the accuracy requirement exceeds error ranges of fault grading.
- Typical fault grading methods:
  - Toggle test, e.g. DATAS
  - Detection probability computation, e.g. STAFAN
  - Fault sampling
    - Estimate from a selected subset of total faults

# Toggle Test



- Circuit node transition
  - is computed during logic simulation and the number of node transition or toggle rate is used as the basis of fault coverage estimation.
  - e.g. **zero toggle rate** implies either s-a-0 or s-a-1 is not detected.
- Only logic simulation is performed.
  - very low computational cost
- Controllability-based estimation
  - Single stuck-at faults are only activated but not necessary propagated to POs.

# STAFAN




- Compute fault detection probability from logic simulation.
  - $d_l$  = detection probability of s-a-0 on  $l$  =  $C1(l)O(l)$
  - $d_l$  = detection probability of s-a-1 on  $l$  =  $C0(l)O(l)$

$$C0(l) = \frac{0\text{-count}}{n}, \quad C1(l) = \frac{1\text{-count}}{n}$$

$$S(l) = \frac{\text{sensitization-count}}{n}$$

$$O(l) = S(l)O(m)$$

 

- $m$  is the immediate successor of  $l$
- **observability** can be computed backwards from POs

# STAFAN(cont.)



- The probability of detecting a fault with  $n$  test vectors

$$d_f^n = 1 - (1 - d_f)^n$$

- $n$  is the # of vectors
- $(1 - d_f)^n$  is prob. of not being detected **after  $n$  test vectors**

- The fault coverage is 
$$\frac{\sum_{f \in \Phi} d_f^n}{|\Phi|}$$

- $\Phi$  is the number of total faults of interests
- More sophisticated than toggle test with same computation complexity



# Fault Sampling




- $M$ : total number of collapsed faults  
 $m$ : number of faults randomly selected  
 $K$ : number of faults detected by the test set  $T$   
 $k$ : number of selected faults detected by  $T$
- Actual fault coverage  $F = K/M$
- $P_k(M, m, K)$ : the probability that  $T$  will detect  $k$  faults from a random sample size of  $m$ , given that it detects  $K$  faults from the entire set of  $M$  faults.



- $$P_k(m, M, K) = \frac{C_k^K C_{m-k}^{M-K}}{C_m^M}$$

 - **$P_k$  is hypergeometric distribution with**  
**mean**  $\mu_k = m K / M = mF$   
**variance**  $\sigma_k^2 = m K / M [1 - k / M] (M - m) / (M - 1)$   
 $\cong mF (1 - F) (1 - m / M)$
- For large  $M$ , this distribution can be approximated by a normal distribution with mean  $\mu_k$  and standard deviation  $\sigma_k$ .



- The estimated fault coverage  $f$  is a random variable with normal distribution:

$$\mu_f = \mu_k / m = F$$

$$\sigma_f^2 = \sigma_k^2 / m^2 = (1/m)F(1-F)(1-m/M)$$

- With a confidence level of 99.7%, the estimated fault coverage  $f \in [F-3\sigma_f, F+3\sigma_f]$ .

$$\begin{aligned} e_{\max} &= 3\sqrt{F(1-F)(1-m/M)1/m} \\ &\cong 3\sqrt{F(1-F)/m} \quad \text{if } m \ll M \end{aligned}$$

Independent of  $M$ !!

# Maximum Errors of the Estimated Fault Coverage

