 


# Chapter 6 Testability Analysis

可測度分析法



# Outline



- Introduction
- SCOAP
- COP
- High-level Testability

# Testability Analysis



- Applications
  - To give early warnings about the test problems
    - Guide the selection of test points to improve testability.
    - Automate the “Design for Testability” problem
  - To provide guidance in ATPG
    - For example, determine the “hardest” & “easiest” inputs in *backtrace* of PODEM
- Complexity should be simpler than ATPG and fault simulation
  - Need to be **linear** or almost linear in terms of circuit size
- Topology analysis
  - Only the **structure** of the circuit is analyzed
  - No test vectors are involved
  - Only an approximation
    - **reconvergent fanouts cause inaccuracy**

# Testability Measures



- Controllability
  - The difficulty of setting a particular logic signal to 0 or 1.
- Observability
  - The difficulty of observing the logic state of a signal.

# SCOAP

## Sandia Controllability/Observability Analysis Program

*Goldstein, DAC 1980*



- SCOAP computes 6 numbers for each node  $N$ .

	0- controllability	1- controllability	Observability
Combinational	$CC^0(N)$	$CC^1(N)$	$CO(N)$
Sequential	$SC^0(N)$	$SC^1(N)$	$SO(N)$

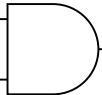
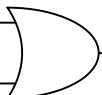

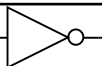
# Combinational SCOAP Measures



- Combinational controllability
  - $CC^0(N)$ ,  $CC^1(N)$
  - Related to the minimum number of combinational node (PI or gate output) assignments required to justify a 0 or 1 on a node  $N$ .
- Combinational observability
  - $CO(N)$
  - Related to the number of gates between  $N$  and PO's, **and**
  - the minimum number of PI assignments required to propagate the logical value on node  $N$  to a primary output.

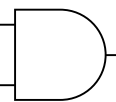
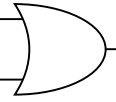
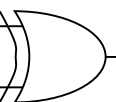
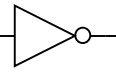

# CC<sup>0</sup>(N) & CC<sup>1</sup>(N)



	CC <sup>0</sup> (y)	CC <sup>1</sup> (y)
$x_1$ $x_2$  $y$	$\min[\text{CC}^0(x_1), \text{CC}^0(x_2)] + 1$	$\text{CC}^1(x_1) + \text{CC}^1(x_2) + 1$
$x_1$ $x_2$  $y$	$\text{CC}^0(x_1) + \text{CC}^0(x_2) + 1$	$\min[\text{CC}^1(x_1), \text{CC}^1(x_2)] + 1$
$x_1$ $x_2$  $y$	$\min[\text{CC}^0(x_1) + \text{CC}^0(x_2), \text{CC}^1(x_1) + \text{CC}^1(x_2)] + 1$	$\min[\text{CC}^0(x_1) + \text{CC}^1(x_2), \text{CC}^1(x_1) + \text{CC}^0(x_2)] + 1$
$x$  $y$	$\text{CC}^1(x) + 1$	$\text{CC}^0(x) + 1$
Primary inputs	1	1

# CO(N)




	$CO(x_1)$
$x_1$ $x_2$  $y$	$CO(y) + CC^1(x_2) + 1$
$x_1$ $x_2$  $y$	$CO(y) + CC^0(x_2) + 1$
$x_1$ $x_2$  $y$	$CO(y) + \min[CC^0(x_2), CC^1(x_2)] + 1$
$x_1$  $y$	$CO(y) + 1$
$x_1$  $y_1$ $y_2$	$\min[CO(y_1), CO(y_2)]$
Primary outputs	0



# An Example – Controllability




$CC^0/CC^1$

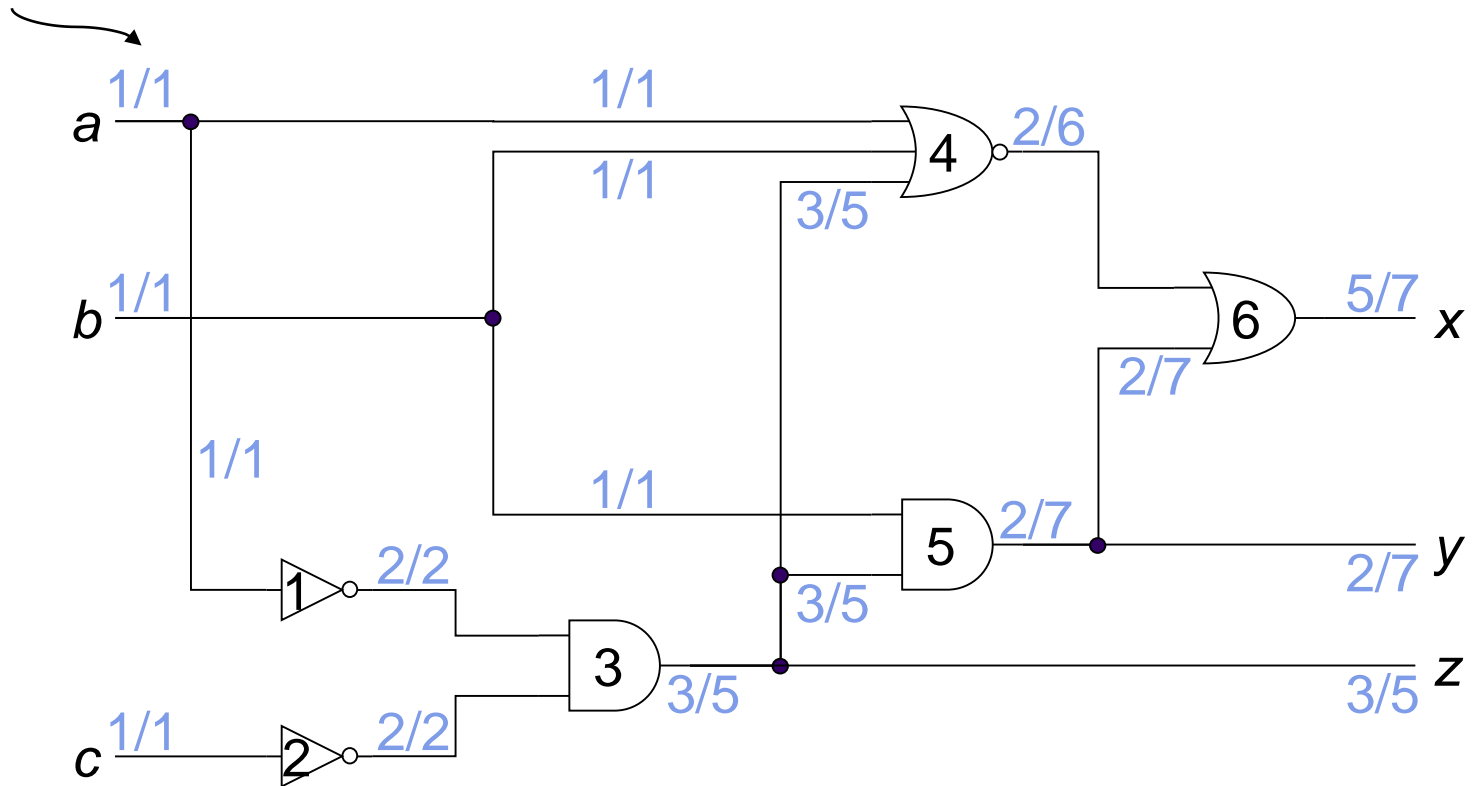

# An Example – Observability



$CC^0/CC^1$

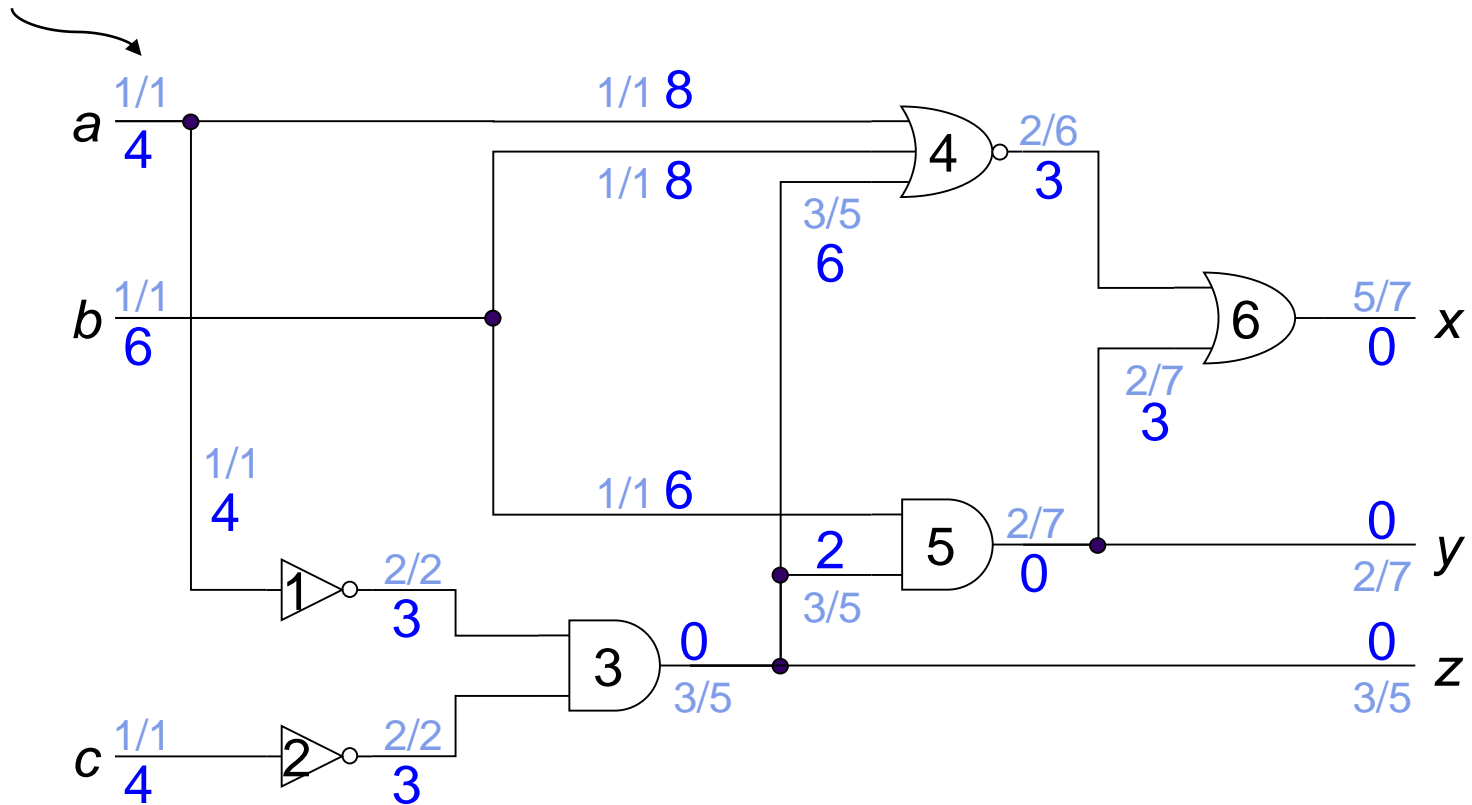

# Sequential SCOAP Measures




- Sequential controllability
  - $SC^0(N)$ ,  $SC^1(N)$
  - Estimate the minimum number of sequential node (FF output) assignments required to justify a 0 or 1 on a node  $N$ .
- Sequential observability
  - $SO(N)$
  - Related to the number of FF's between  $N$  and PO's, **and**
  - the minimum number of FF assignments required to propagate the logical value on node  $N$  to a primary output.





# Computing the Sequential SCOAP Measures



- **Computation of  $SC^0(N)$ ,  $SC^1(N)$ , and  $SO(N)$  is similar to that of  $CC^0(N)$ ,  $CC^1(N)$ , and  $CO(N)$ .**
- **The differences are**
  - One increments the sequential measures by 1 only when signals propagate from FF inputs to Q or Q', or backwards.
  - Several iterations may be required for the controllability numbers to converge.






# Computing $SC^0(N)$ and $SC^1(N)$

 

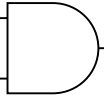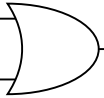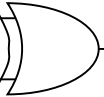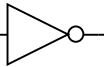
	$SC^0(y)$	$SC^1(y)$
$x_1$ $x_2$  $y$	$\min[SC^0(x_1), SC^0(x_2)]$	$SC^1(x_1) + SC^1(x_2)$
$x_1$ $x_2$  $y$	$SC^0(x_1) + SC^0(x_2)$	$\min[SC^1(x_1), SC^1(x_2)]$
$x_1$ $x_2$  $y$	$\min[SC^0(x_1) + SC^0(x_2), SC^1(x_1) + SC^1(x_2)]$	$\min[SC^0(x_1) + SC^1(x_2), SC^1(x_1) + SC^0(x_2)]$
$x$  $y$	$SC^1(x)$	$SC^0(x)$
Primary inputs	0	0

# SO(N)

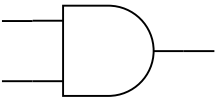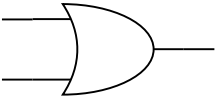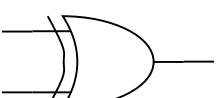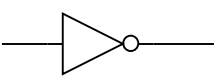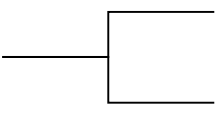


	$SO(x_1)$
$x_1$ $x_2$  $y$	$SO(y) + SC^1(x_2)$
$x_1$ $x_2$  $y$	$SO(y) + SC^0(x_2)$
$x_1$ $x_2$  $y$	$SO(y) + \min[SC^0(x_2), SC^1(x_2)]$
$x_1$  $y$	$SO(y)$
$x_1$  $y_1$ $y_2$	$\min[SO(y_1), SO(y_2)]$
Primary outputs	0

# Flip-Flop

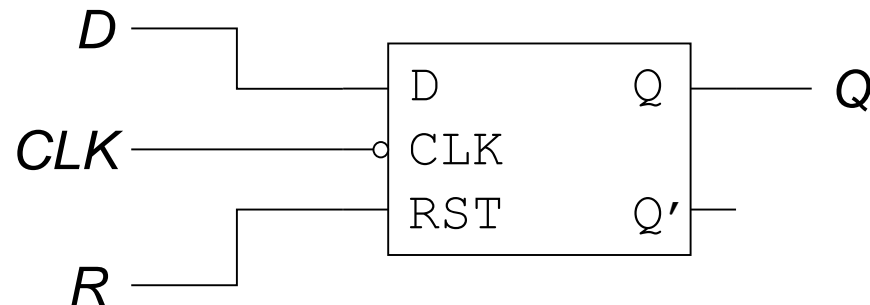

$$\begin{aligned} CC^1(Q) &= CC^1(D) + CC^1(CLK) + CC^0(CLK) + CC^0(R) \\ SC^1(Q) &= SC^1(D) + SC^1(CLK) + SC^0(CLK) + SC^0(R) + 1 \end{aligned}$$
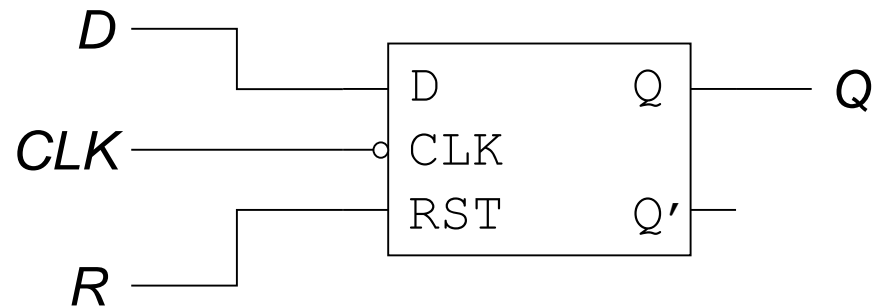
$$\begin{aligned} CC^0(Q) &= \min[CC^1(R) + CC^0(CLK), \\ &\quad CC^0(D) + CC^1(CLK) + CC^0(CLK) + CC^0(R)] \\ SC^0(Q) &= \min[SC^1(R) + SC^0(CLK), \\ &\quad SC^0(D) + SC^1(CLK) + SC^0(CLK) + SC^0(R)] + 1 \end{aligned}$$



$$\begin{aligned} CO(D) &= CO(Q) + CC^1(CLK) + CC^0(CLK) + CC^0(R) \\ SO(D) &= SO(Q) + SC^1(CLK) + SC^0(CLK) + SC^0(R) + 1 \end{aligned}$$




# Computing Testability Measures for Sequential Circuits




1. For all PI's, set  $CC^0 = CC^1 = 1$  and  $SC^0 = SC^1 = 0$ .
2. For all other nodes, set  $CC^0 = CC^1 = \infty$  and  $SC^0 = SC^1 = \infty$ .
3. Propagate controllability measures from PI's to PO's.  
Iterate until the controllability numbers stabilize.
4. For all PO's, set  $CO = SO = 0$ .
5. For all other nodes, set  $CO = SO = \infty$ .
6. Propagate observability from PO's to PI's.

# Controllability Computation

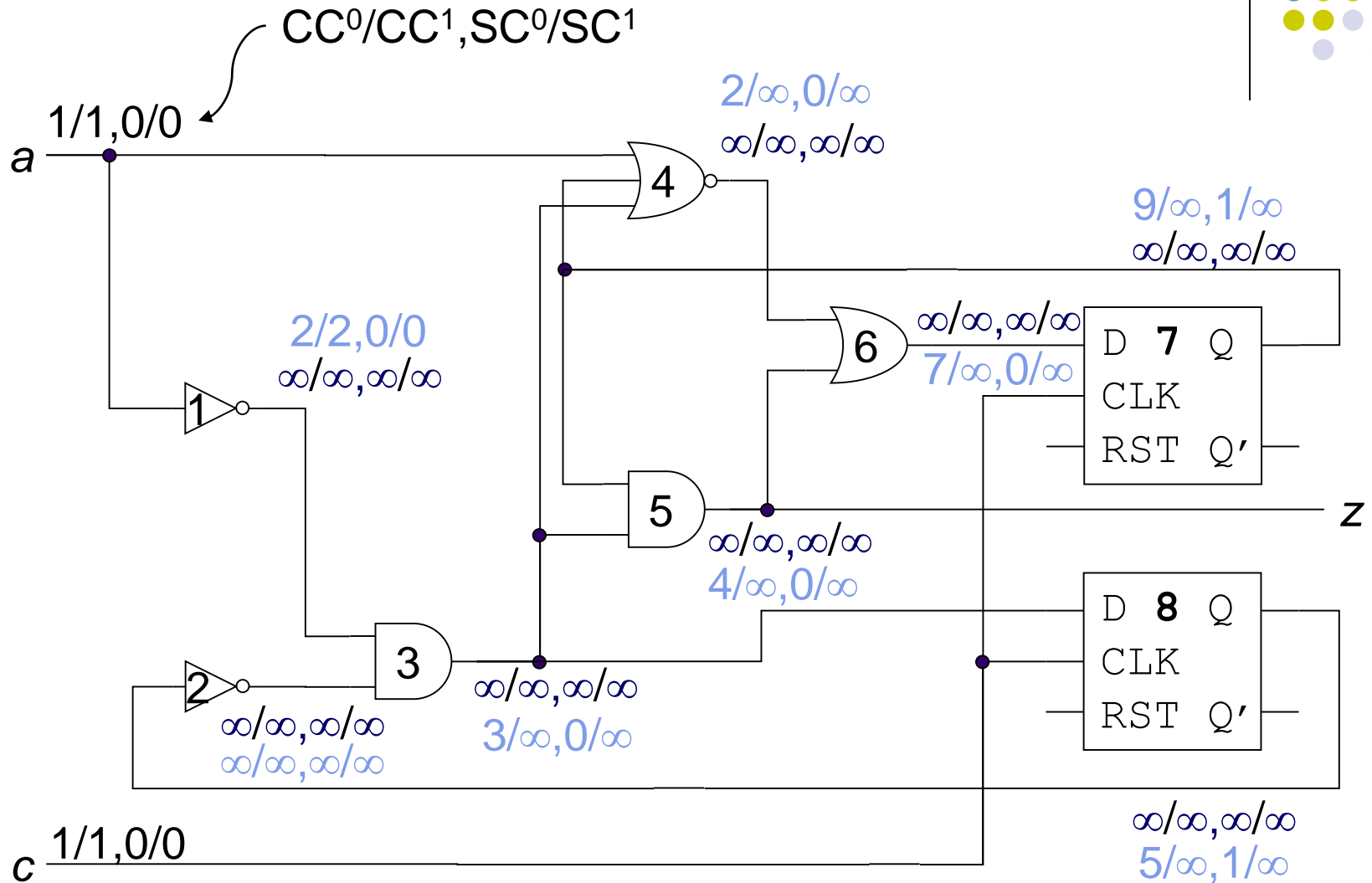


Assuming no RST can occur

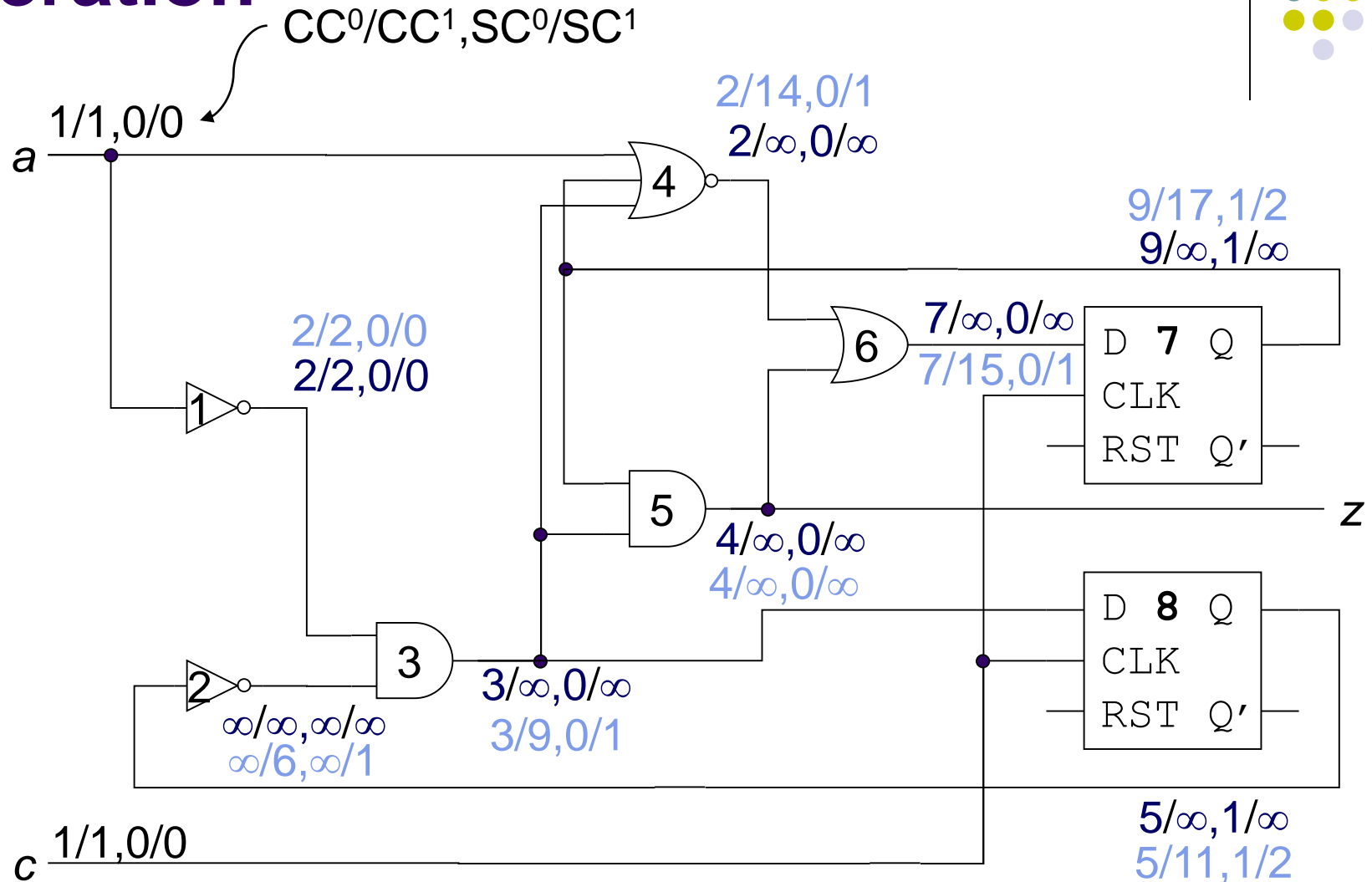
# Controllability Computation – 2nd Iteration


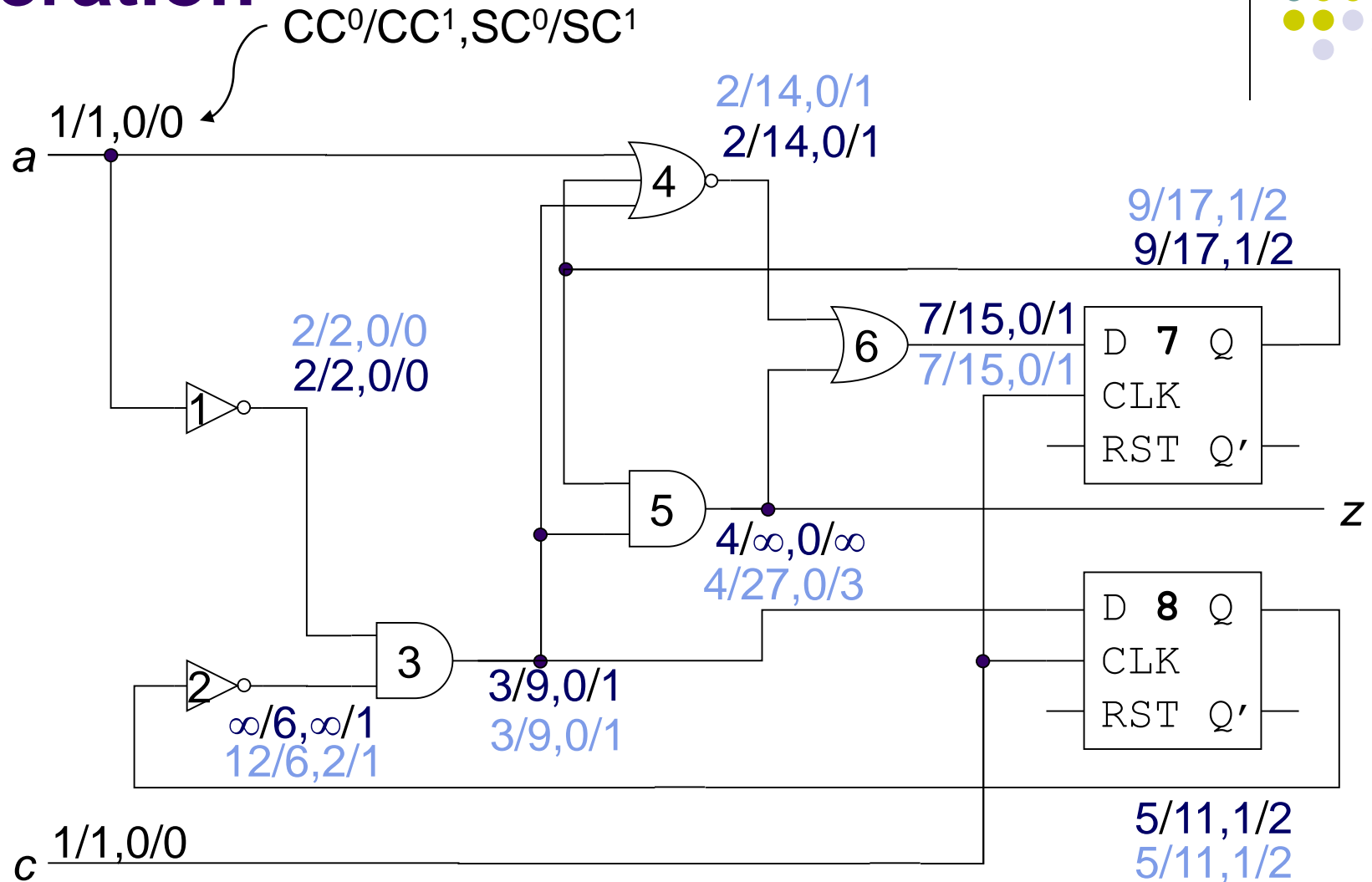
# Controllability Computation – 3rd iteration






# Observability Computation

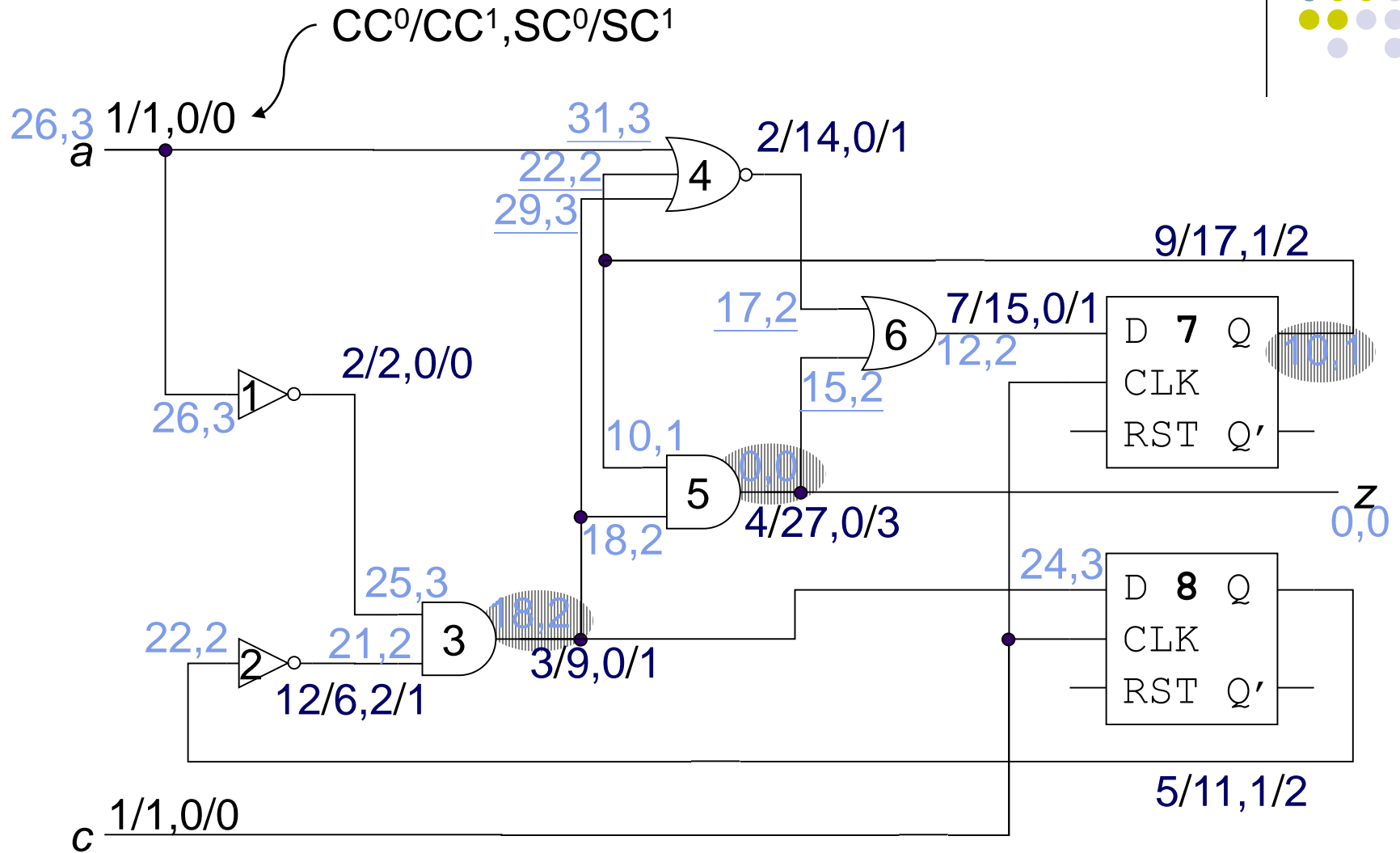

# COP [F. Brglez, '84]




- $C_x$ : the probability of  $x$  being 1.
- $O_x$ : the probability of  $x$  being observed at a PO.

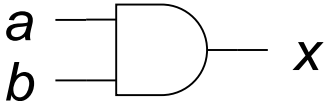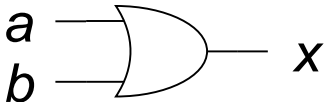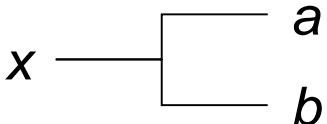	$C_x$	$O_a$
	$C_x = C_a \times C_b$	$O_a = O_x \times C_b$
	$C_x = 1 - (1 - C_a) \times (1 - C_b)$	$O_a = O_x \times (1 - C_b)$
	$C_x = C_a = C_b$	$O_x = 1 - (1 - O_a) \times (1 - O_b)$


# An Example – Controllability



COP values

 


Actual contrallabilities

 


# An Example – Observability



COP values

 

Actual observabilities

 



# PODEM: Example (1/3)




Initial objective=(G5,1).

G5 is an AND gate → Choose the hardest-1

→ Back-trace to (G1,1).

G1 is an AND gate → Choose the hardest-1

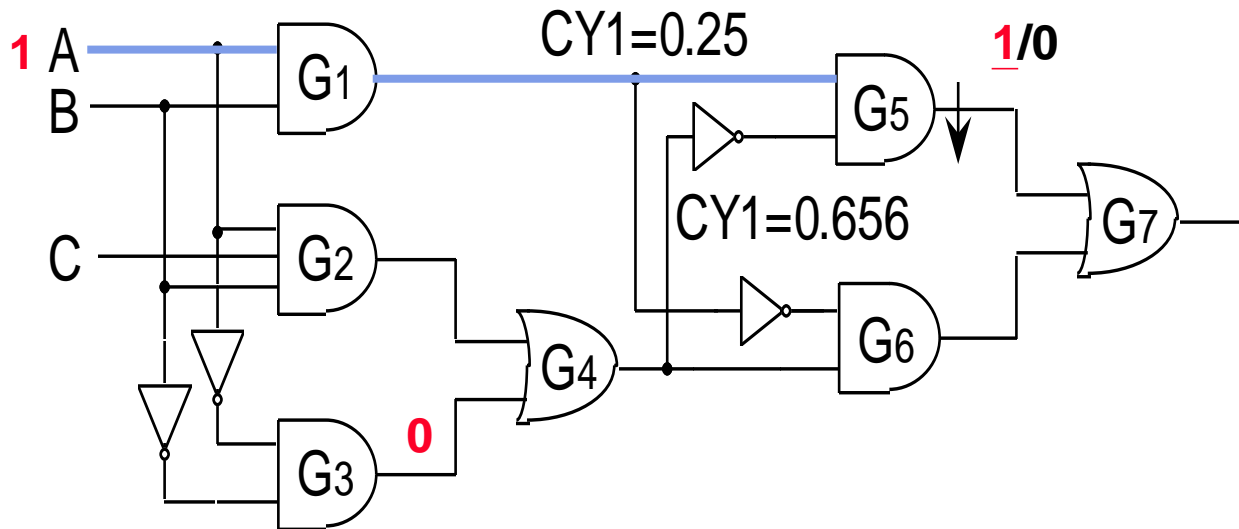→ Arbitrarily, back-trace to (A,1). A is a PI → Implication → G3=0.




The diagram shows a logic circuit for a 3-input majority gate. The inputs are A, B, and C. The circuit is composed of seven gates: G1 (AND), G2 (AND), G3 (AND), G4 (OR), G5 (AND), G6 (AND), and G7 (OR). The inputs are A=1, B=1, and C=0. The circuit is annotated with values: CY1=0.25 for G1, CY1=0.656 for G5, and a final output of 1/0. A blue line highlights the path from B through G1 and G5.
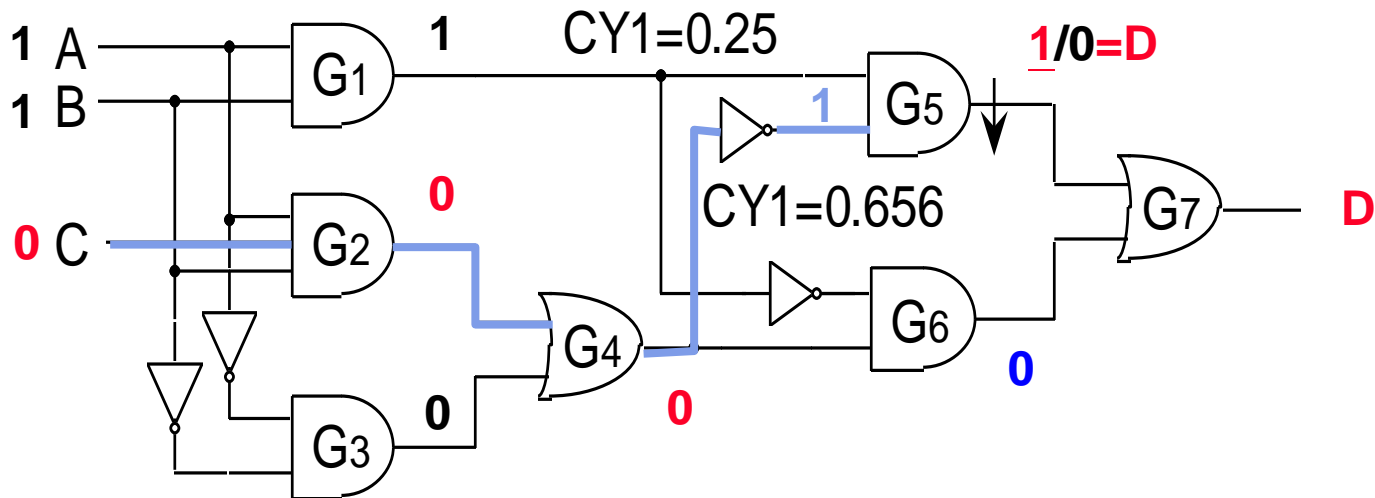
# PODEM: Example (3/3)



The initial objective satisfied? No! → **Current objective=(G5,1).**  
The value of G1 is known → **Back-trace to (G4,0).**  
The value of G3 is known → **Back-trace to (G2,0).**  
A, B is known → **Back-trace to (C,0).**  
C is a PI → Implication → **G2=0, G4=0, G5=D, G7=D.**



**No backtracking !!**

# If The Backtracing Is Not Guided (1/3)




Initial objective=(G5,1).

Choose path G5-G4-G2-A  $\rightarrow A=0$ .

Implication for  $A=0 \rightarrow G1=0$ ,  $G5=0 \rightarrow$  Backtracking to  $A=1$ .

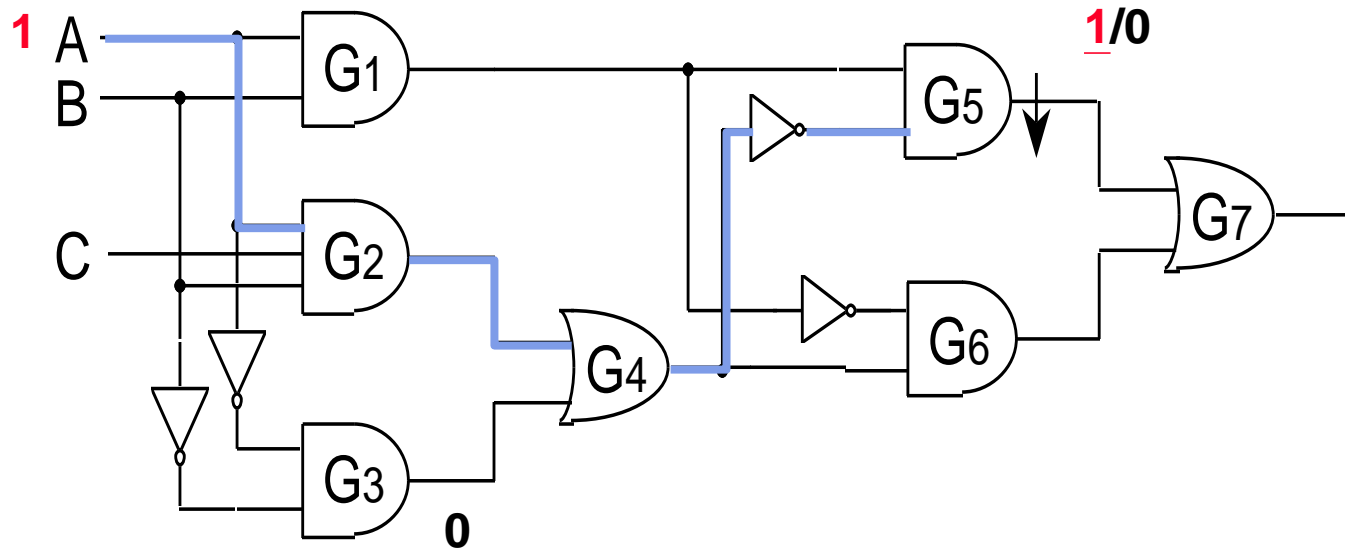
Implication for  $A=1 \rightarrow G3=0$ .


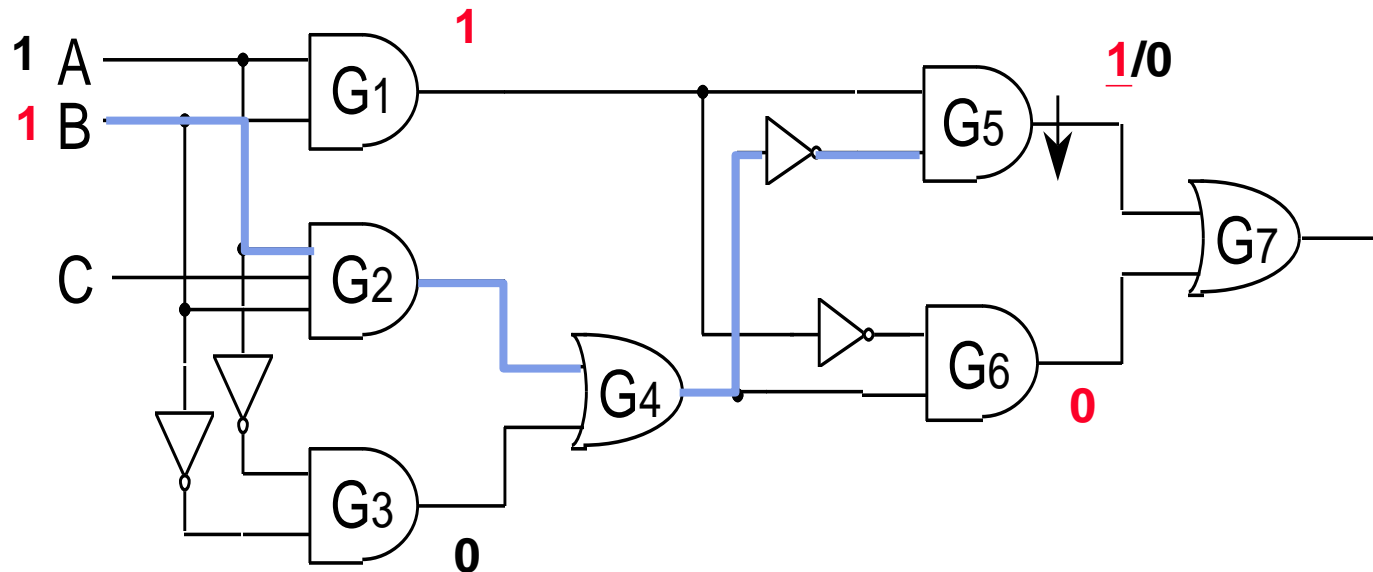
# If The Backtracing Is Not Guided (2/3)





The initial objective satisfied? No! → **Current objective=(G5,1).**  
Choose path G5-G4-G2-B → **B=0.**  
Implication for B=0 → G1=0, G5=0 → **Backtracking to B=1.**  
Implication for B=1 → G1=1, G6=0.


 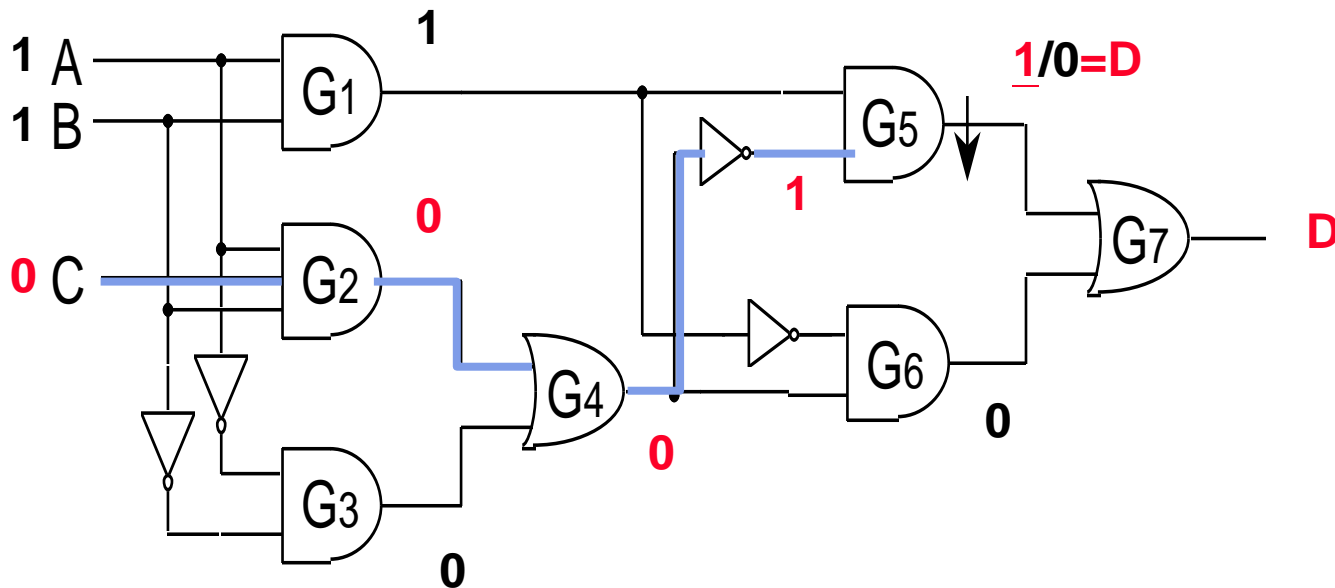
# If The Backtracing Is Not Guided (3/3)




The initial objective satisfied? No!  $\rightarrow$  Current objective=(G5,1).  
Choose path G5-G4-G2-C  $\rightarrow$  **C=0**.  
Implication for **C=0**  $\rightarrow$  G2=0, G4=0, G5=D, G7=D.



**Two times of backtracking !!**

# High-Level Testability Analysis


 


- **Based on behavioral level circuit model.**
- **Usually part of the behavior synthesis program.**
- **To improve the testability at earlier design stage.**
  
# Data Flow Graph (DFG)



- Each node corresponds to a register.
- Each arc represents a combinational path between two registers.





 
# A High-Level Testability Measure – Sequential Depth



- The length of a sequential path between two nodes is the number of arcs along the path.
- The sequential depth between a pair of registers is the length of the shortest path between them.



$R1 \rightarrow R1 : 0$

$R2 \rightarrow R1 : 1$

$R3 \rightarrow R1 : 2$

$R4 \rightarrow R1 : 2$

$a \rightarrow g : 2$

$b \rightarrow g : 3$


$d \rightarrow g : 4$

$e \rightarrow g : 4$
 
# Testability Enhancement








- Improve controllability and observability of registers.
  - Whenever possible, allocate a register to at least one PI or PO.
- Reduce the sequential depth between a controllable and an observable registers.




R1 → R1 : 0  
R2 → R1 : 1  
R3 → R1 : 2  
R4 → R1 : 2

# An Example

  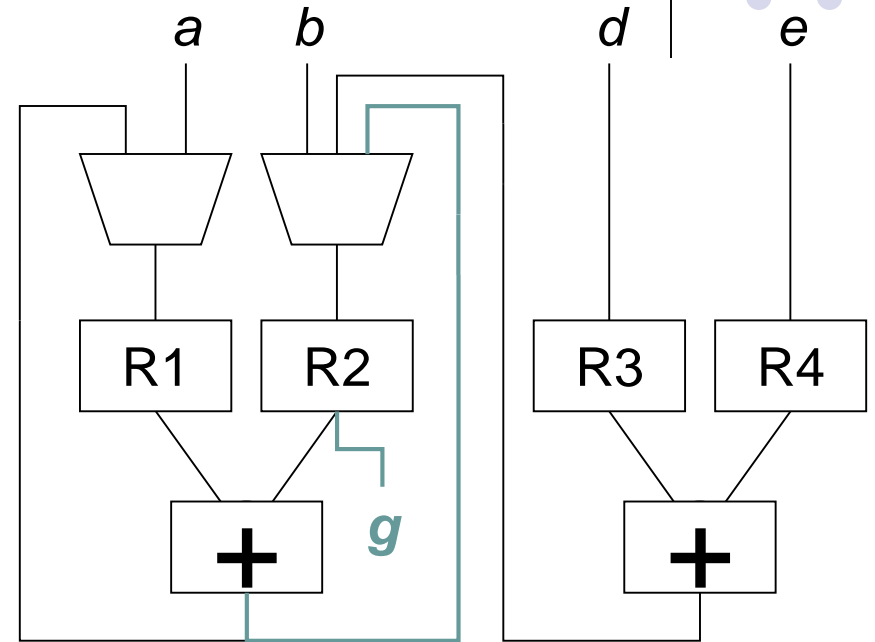 

 

 $R1 \rightarrow R1 : 0$   
 $R2 \rightarrow R1 : 1$   
 $R3 \rightarrow R1 : 2$   
 $R4 \rightarrow R1 : 2$



$R1 \rightarrow R2 : 1$   
 $R2 \rightarrow R2 : 0$   
 $R3 \rightarrow R2 : 1$   
 $R4 \rightarrow R2 : 1$

